



Electrical Circuits

Series dc Circuits

By



Hilal Talib Yaseen

الأفكار المركزية

- 1- connection and series CSC**
- 2 – current in series circuits**
- 3 - voltage in series circuits**
- 4- Total Resistance for series circuits**
- 5 - Total power in series circuits**
- 6 – Voltage divider**
- 7 – Examples and Homeworks**

Series Connection of Resistors

Here's How Resistors Add in Series

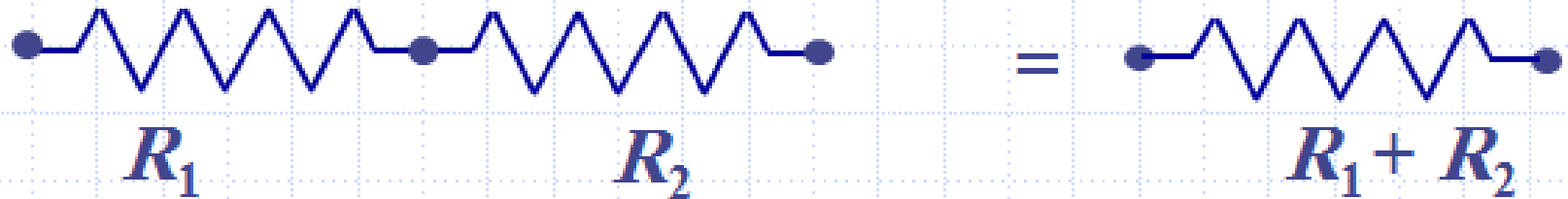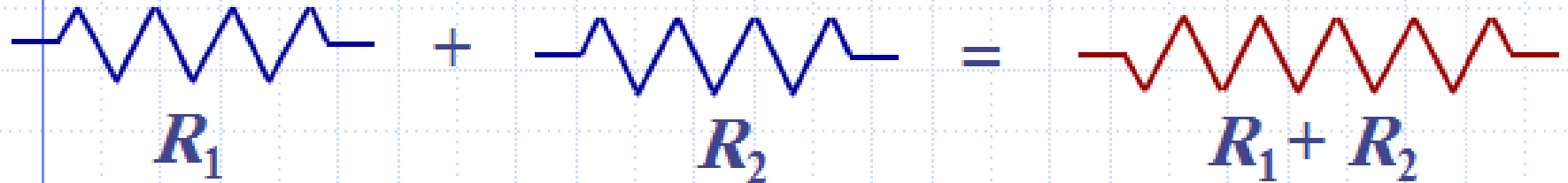

Equivalent Resistance

Q1- Write Series connection csc

- 1- Same current is flow in all Resistances it $=i_1=i_2$
- 2- Voltage is shared between the Resistances
- 3 – Voltage across each Resistor is given by ohm ,s Law
 $V = IR$
- 4- Total voltage is equal to the sum of voltage s
 $E = V_1 + V_2 +$
- 5- Total Resistance is the sum of series Resistances
- 6- Total power is the sum of powers in each Resistor

Series CSC.

5- Total Resistance is the sum of series Resistances

$$R_t = R_1 + R_2 + R_3$$

6- For equal Resistors $R_t = N R$


7 - The smaller the Resistor , the smaller voltage drop

6- Total power is the sum of powers in each Resistor

1 - Same current flow in the circuit ($I_1 = I_2 = I$)


SERIES CIRCUIT

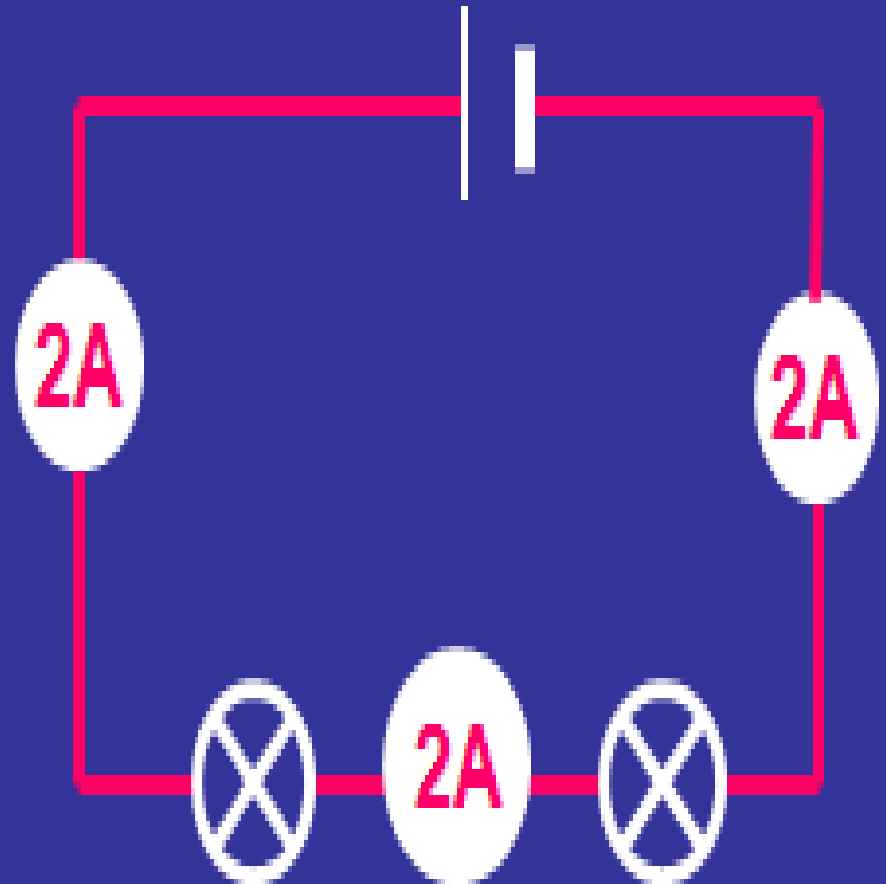- current is the **same** at all points in the circuit.



2A--Voltage is distributed between the components ($E = V1 + V2$)

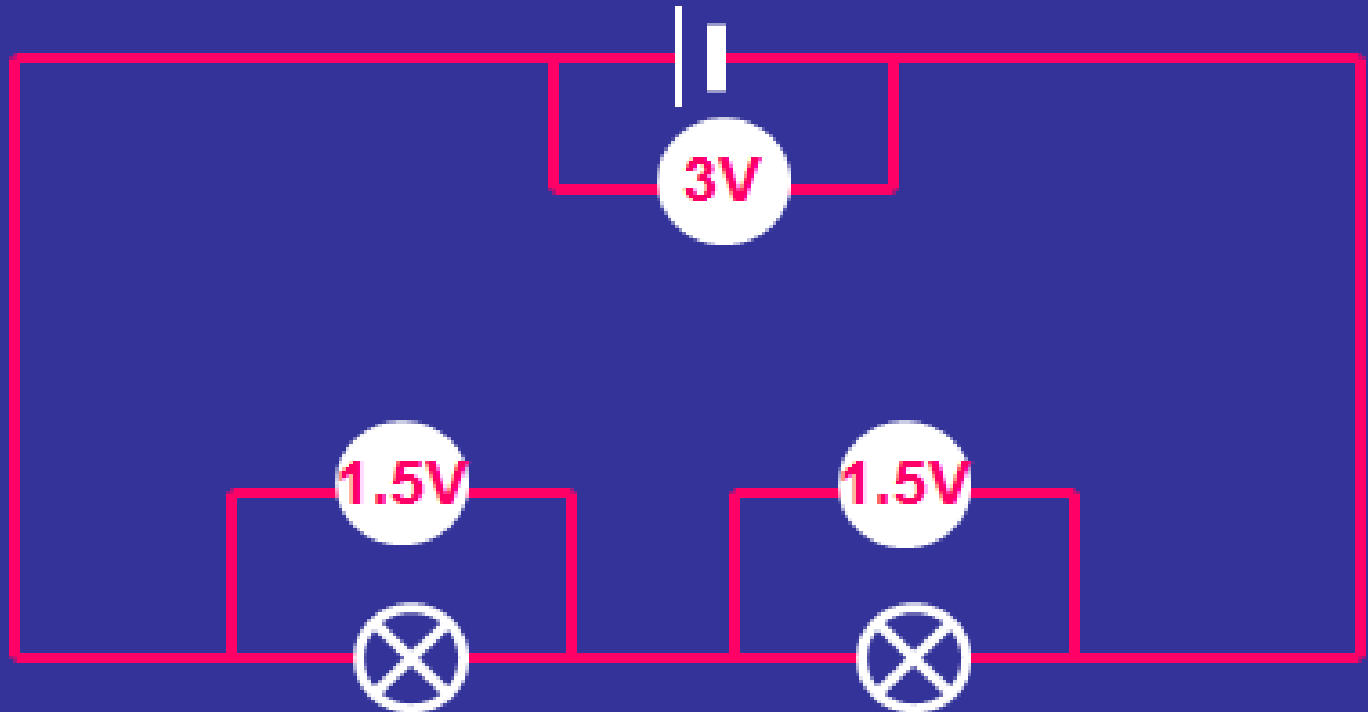- voltage is **shared** between the components



2 B – Voltage across a resistors is given by ohm,s law

$$V_1 = IR_1 \quad V_2 = IR_2 \quad V_3 = IR_3$$

⚡ The polarity of the voltage across a resistor is determined by the direction of the current

3 - The total resistance of a series configuration is the sum of the resistance level.

$$R_T = R_1 + R_2 + R_3 + R_4 + \dots + R_N$$

4 - Series Resistors

⌘ When series resistors have the same value,

$$R_T = NR$$

⌘ Where N = the number of resistors in the string.

5 - Power Distribution in a Series Circuit

⌘ The power applied by the dc supply must equal that dissipated by the resistive elements.

$$P_E = P_{R_1} + P_{R_2} + \dots + P_{R_N}$$

$$P_1 = V_1 I_1 = I^2 R_1 = \frac{V_1^2}{R_1}$$

$$P_2 = V_2 I_2 = I^2 R_2 = \frac{V_2^2}{R_2}$$

$$P_t = V I = I^2 R_t$$

6 – Voltage Division in a Series Circuit

- ⌘ The voltage across the resistive elements will divide as the magnitude of the resistance levels.
 - ⌘ The greater the value of a resistor in a series circuit, the more of the applied voltage it will capture.
- ⌘ Voltage Divider Rule (VDR)
 - ⌘ The VDR permits determining the voltage levels of a circuit without first finding the current.

$$V_X = R_X \frac{E}{R_T}$$

Problem 1. For the circuit shown in Fig. 5.2, determine (a) the battery voltage V , (b) the total resistance of the circuit, and (c) the values of resistors R_1 , R_2 and R_3 , given that the p.d.'s across R_1 , R_2 and R_3 are 5 V , 2 V and 6 V respectively.

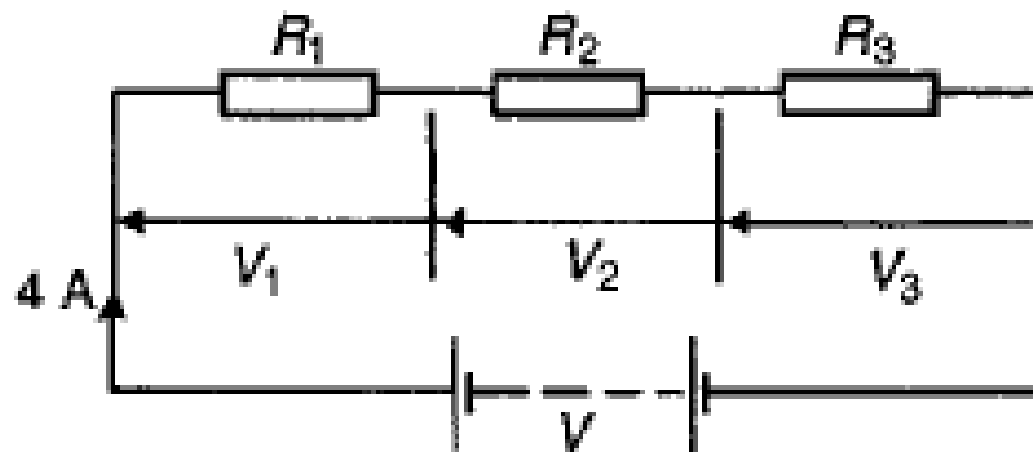


Figure 5.2

(a) Battery voltage $V = V_1 + V_2 + V_3$
 $= 5 + 2 + 6 = 13 \text{ V}$

(b) Total circuit resistance $R = \frac{V}{I} = \frac{13}{4} = 3.25 \Omega$

(c) Resistance $R_1 = \frac{V_1}{I} = \frac{5}{4} = 1.25 \Omega$

Resistance $R_2 = \frac{V_2}{I} = \frac{2}{4} = 0.5 \Omega$

Resistance $R_3 = \frac{V_3}{I} = \frac{6}{4} = 1.5 \Omega$

(Check: $R_1 + R_2 + R_3 = 1.25 + 0.5 + 1.5 = 3.25 \Omega = R$)

Problem 2. For the circuit shown in Fig. 5.3, determine the p.d. across resistor R_3 . If the total resistance of the circuit is $100\ \Omega$, determine the current flowing through resistor R_1 . Find also the value of resistor R_2 .

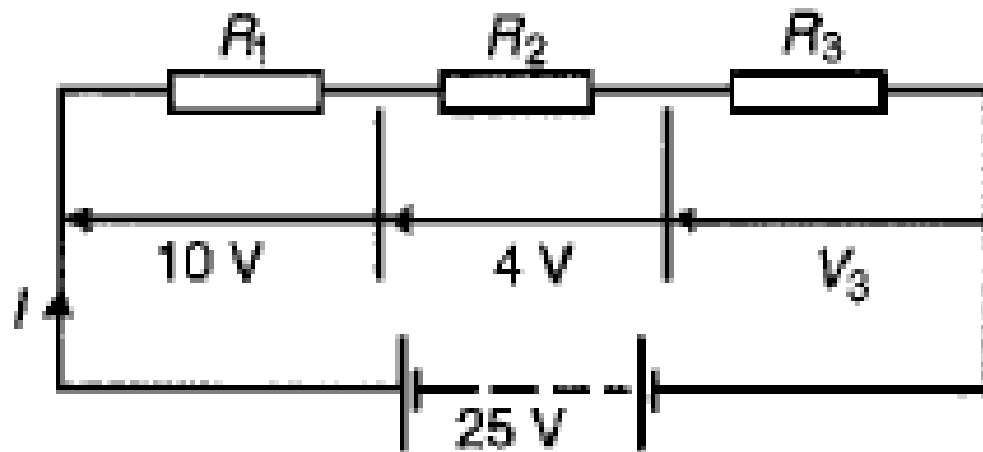


Figure 5.3

P.d. across R_3 , $V_3 = 25 - 10 - 4 = 11 \text{ V}$

$$\text{Current } I = \frac{V}{R} = \frac{25}{100} = 0.25 \text{ A,}$$

which is the current flowing in each resistor

$$\text{Resistance } R_2 = \frac{V_2}{I} = \frac{4}{0.25} = 16 \Omega$$

Problem 3. A 12 V battery is connected in a circuit having three series-connected resistors having resistance's of $4\ \Omega$, $9\ \Omega$ and $11\ \Omega$. Determine the current flowing through, and the p.d. across the $9\ \Omega$ resistor. Find also the power dissipated in the $11\ \Omega$ resistor.

The circuit diagram is shown in Fig. 5.4

Total resistance $R = 4 + 9 + 11 = 24 \Omega$

$$\text{Current } I = \frac{V}{R} = \frac{12}{24} = 0.5 \text{ A,}$$

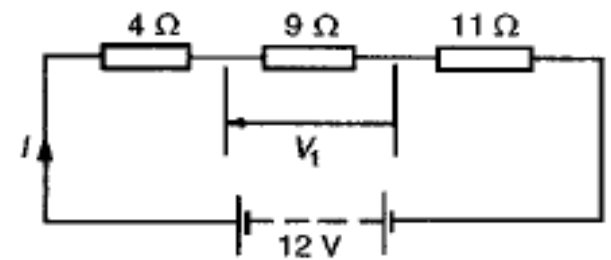


Figure 5.4

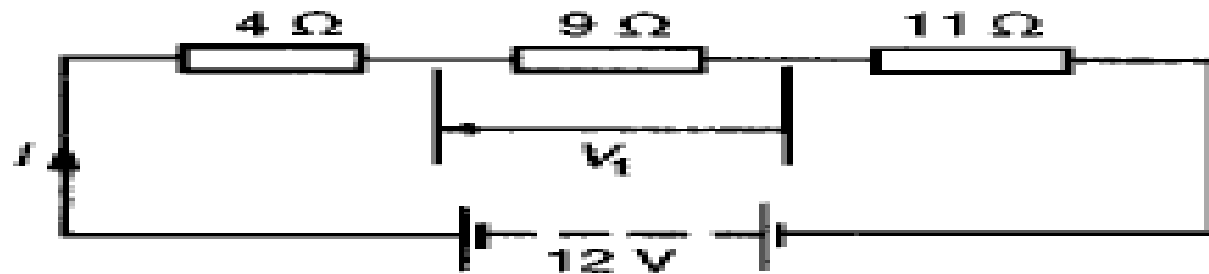


Figure 5.4


which is the current in the 9Ω resistor.
P.d. across the 9Ω resistor,

$$V_1 = I \times 9 = 0.5 \times 9 = 4.5 \text{ V}$$

Power dissipated in the 11Ω resistor,

$$\begin{aligned} P &= I^2 R = (0.5)^2 (11) \\ &= (0.25)(11) = 2.75 \text{ W} \end{aligned}$$

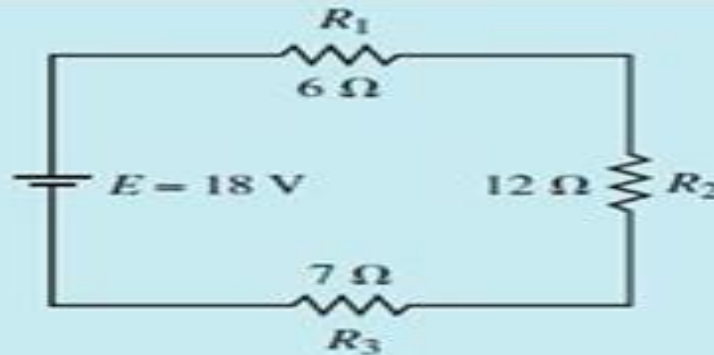Example – 4 For the ckt find voltage drops across each resistor



Solution

$$R_T = 6\ \Omega + 12\ \Omega + 7\ \Omega = 25.0\ \Omega$$

$$V_1 = \left(\frac{6\ \Omega}{25\ \Omega}\right)(18\ \text{V}) = 4.32\ \text{V}$$

$$V_2 = \left(\frac{12\ \Omega}{25\ \Omega}\right)(18\ \text{V}) = 8.64\ \text{V}$$

$$V_3 = \left(\frac{7\ \Omega}{25\ \Omega}\right)(18\ \text{V}) = 5.04\ \text{V}$$

The total voltage drop is the summation

$$V_T = 4.32\ \text{V} + 8.64\ \text{V} + 5.04\ \text{V} = 18.0\ \text{V} = E$$

Problem 5. Two resistors are connected in series across a 24 V supply and a current of 3 A flows in the circuit. If one of the resistors has a resistance of $2\ \Omega$ determine (a) the value of the other resistor, and (b) the p.d. across the $2\ \Omega$ resistor. If the circuit is connected for 50 hours, how much energy is used?

The circuit diagram is shown in Fig. 5.8

(a) Total circuit resistance

$$R = \frac{V}{I} = \frac{24}{3} = 8 \Omega$$

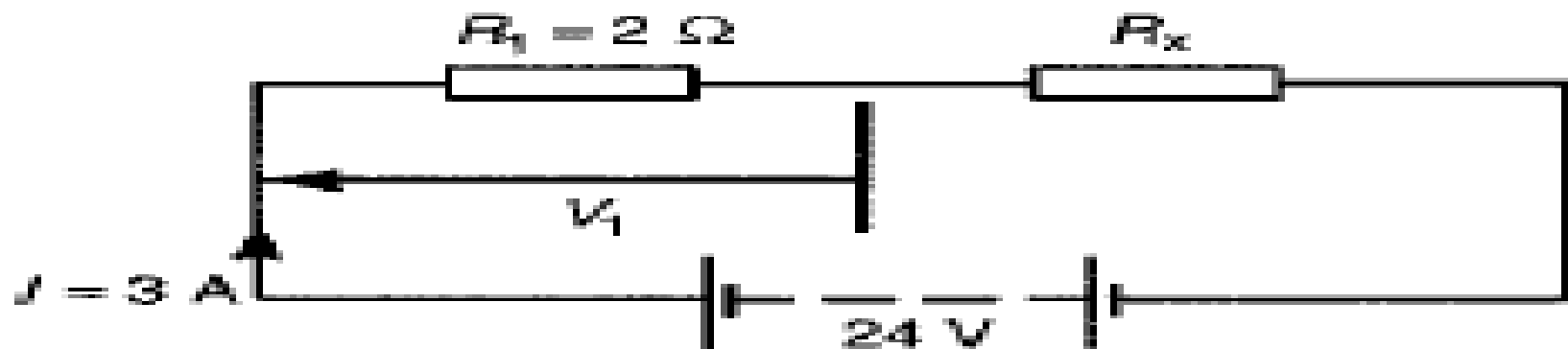


Figure 5.8

Value of unknown resistance,

$$R_x = 8 - 2 = 6 \Omega$$

(b) P.d. across 2Ω resistor,

$$V_1 = IR_1 = 3 \times 2 = 6 \text{ V}$$

Alternatively, from above,

$$\begin{aligned} V_1 &= \left(\frac{R_1}{R_1 + R_x} \right) V \\ &= \left(\frac{2}{2 + 6} \right) (24) = 6 \text{ V} \end{aligned}$$

Energy used = power \times time

$$= (V \times I) \times t$$

$$= (24 \times 3 \text{ W})(50 \text{ h})$$


$$= 3600 \text{ Wh} = 3.6 \text{ kWh}$$

Example - 6 find the voltage drops across each resistor by using VDR

Solution:

$$V_1 = \frac{R_1 E}{R_T} = \frac{(2 \text{ k}\Omega)(45 \text{ V})}{2 \text{ k}\Omega + 5 \text{ k}\Omega + 8 \text{ k}\Omega} = \frac{(2 \text{ k}\Omega)(45 \text{ V})}{15 \text{ k}\Omega}$$
$$= \frac{(2 \times 10^3 \Omega)(45 \text{ V})}{15 \times 10^3 \Omega} = \frac{90 \text{ V}}{15} = 6 \text{ V}$$
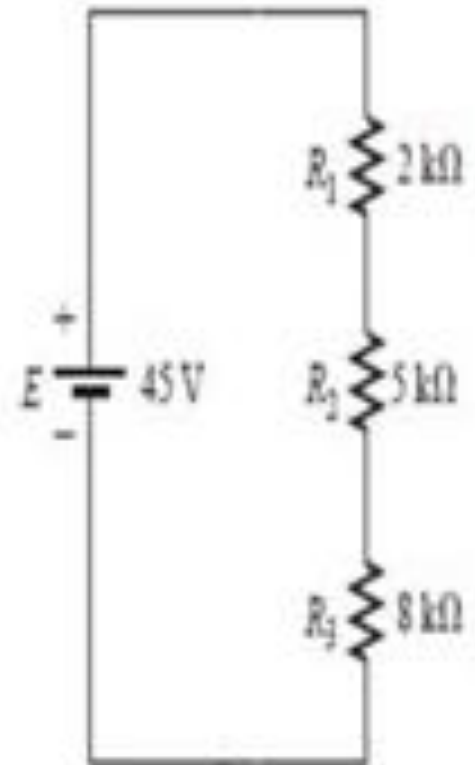
$$V_3 = \frac{R_3 E}{R_T} = \frac{(8 \text{ k}\Omega)(45 \text{ V})}{15 \text{ k}\Omega} = \frac{(8 \times 10^3 \Omega)(45 \text{ V})}{15 \times 10^3 \Omega}$$
$$= \frac{360 \text{ V}}{15} = 24 \text{ V}$$



Example :

Three Resistances $R_1 = 2k\ \Omega$, $R_2 = 5\ k\Omega$, $R_3 = 8\ k\Omega$
are connected in series to $E = 45\ V$ supply Use voltage
divider law determine the voltage V_1 , V_2 , V_3

Solution :

$$R_t = 2k + 5k + 8k = 15\ k\Omega$$

$$V_1 = \frac{R_1}{R_t} E = \frac{2k}{15k} * 45 = 6V$$

$$V_2 = \frac{R_2}{R_t} E = \frac{5k}{15k} * 45 = 15V$$

$$V_3 = \frac{R_3}{R_t} E = \frac{8k}{15k} * 45 = 24\ V$$

Example :

Two resistors $R_1 = 4 \Omega$ $R_2 = 6 \Omega$ are connected in series to supply 20 v calculate

1 – Total Resistance

2 – Total Current

3 – Voltage across each resistor

4 – Total Power

$$1 - \underline{R_t} = R_1 + R_2 = 4 + 6 = 10\Omega$$

$$2 - I_t = \frac{V}{R_t} = \frac{20}{10} = 2A$$

$$3 - V_1 = I R_1 = 2 * 4 = 8 V$$

$$V_2 = I R_2 = 2 * 6 = 12 V$$

$$4 - P_1 = I^2 R_1 = 2^2 * 4 = 4 * 4 = 16 W$$

$$P_2 = I^2 R_2 = 2^2 * 6 = 4 * 6 = 24 W$$

$$P_t = p_1 + p_2 = 16 + 24 = 40 w$$

$$P_t = I^2 R_t = 2^2 * 10 = 4 * 10 = 40 w$$

Example : 9

H.W

four resistors 5 , 10 , 15 , 20 Ω are connected in series to (100 v) supply determine

1 – Total Resistance

2 – Total current

3 – voltage drop across each resistor

4 - Total Power consumed

5 – Total Power delivered

Example : 10 (H.W)

For the circuit shown in Fig. 5.9, determine the value of V_1 . If the total circuit resistance is 36Ω determine the supply current and the value of resistors R_1 , R_2 and R_3

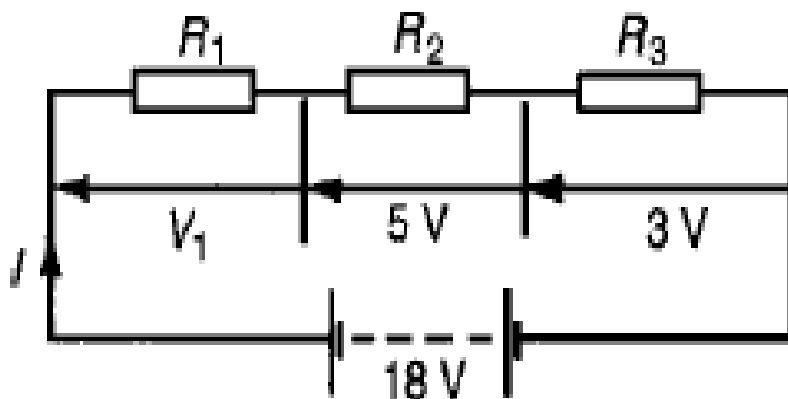


Figure 5.9

Example :11-When the switch in the circuit (5-10) is closed the reading on voltmeter 1 is 30 v and that on voltmeter 2 is 10 v Determine the reading on the ammeter and the value of resistor R2 (H.W)

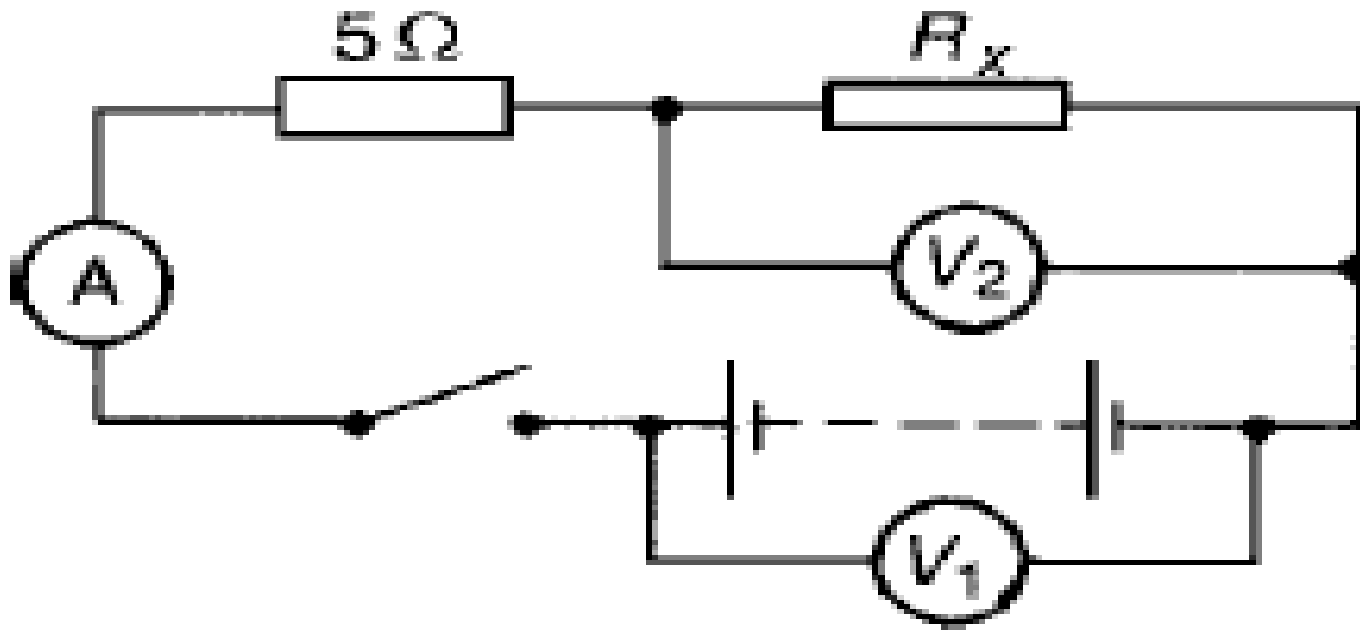


Figure 5.10