<u>Week No</u>- 3

- Using the transistor as a switch
- Regions of operation
- Switch(cutoff and saturation)



Transistors

Power Electronic devices that can switch on or off

- Power Transistors (BJT)
- IGBTs
- MOSFETs

The **IGBT** is now the most commonly used for drives

Bipolar Junction Transistor(BJT):

- The BJT is the most common transistor.
- It consists of three sections of semiconductors: an emitter, a base and a collector.
- In an npn-type BJT, the emitter and the collector are made of n-type semiconductors and the base is made of a p-type semiconductor

Transistor Characteristics and Parameters

There are three key dc voltages and three key dc currents to be considered.Note that these measurements are important for troubleshooting.

*I*_B:dc base current

*I*_E:dc emitter current

*I*_c:dc collector current

V_{BE}:dc voltage across baseemitter junction

V_{CB}:dc voltage across collector-base junction

V_{CE}:dc voltage from Collector to emitter



Active	Saturation	Cut-off
region	region	region
 IE increased, Ic increased BE junction forward bias and CB junction reverse bias Refer to the graf, Ic ≈ IE Ic not depends on Vcв Suitable region for the transistor working as amplifier 	 BE and CB junction is forward bias Small changes in VcB will cause big different to Ic The allocation for this region is to the left of VcB = 0 V. 	 Region below the line of IE=0 A BE and CB is reverse bias no current flow at collector, only leakage current

Diode Model of the npn BJT

- The diode is controlled by the voltage at B.
- When the diode is completely on, the switch is closed. This is the saturation region.
- When the diode is completely off, the switch is open. This is the cutoff region.
- When the diode is in between we are in the active region.



npn Common Emitter Characteristics



I –V output characteristics of BJT



Common Emitter configuration

EXAMPLE

Design the transistor switching circuit shown in Figure



Step1. Calculate the collector current when the bulb is in the on state. The supply voltage is divided by the resistance of the load (bulb).

$$I_c = I_L = V_{cc}/R_L = 12V/10 \ \Omega = 1.2A$$

Step2. Using beta, calculate the needed base current.

$$I_{B} = I_{C} / \beta = 1.2A / 100 = 12mA$$

Step3. Calculate the value of V_{RB} .

$$V_{RB} = V_{control} - V_{BE} = 5V - 0.7V = 4.3V$$

Step4. Calculate the value of R_b.

 $R_b = V_R B/I_B = 4.3V/12 \text{ mA} = 358\Omega$ (Use the next lower standard value, 330 Ω .)

Step5. Draw the switching circuit.(The switching circuit is shown in Figure.)

Using the transistor as a switch





Saturation

- Transistor saturation can be guaranteed by designing the circuit so that: $-+V_{pk}=V_{CC}$
 - $-I_B$ is greater than $I_{C(sat)}/h_{FE}$



BJT Switching Times





Lesson Summary

- A Bipolar Junction Transistor is a minority carrier, current controlled unidirectional device.
- A BJT can be of n-p-n or p-n-p type with three terminals called the collector, the base and the emitter.
- A BJT can operate in cut-off, active or saturation regions.
- In the cut-off region the base emitter junction is reverse biased and the collector current is almost zero.
- In the active region the ratio of collector current to base current is fairly constant. This ratio is called the dc current gain (β).
- A transistor can be driven into saturation by increasing the base current For a given collector current. In saturation the V_{cE} voltage drop of a transistor is very low.