



# **Electrical circuits**

## **Parallel dc Circuits**


by  
Hilal talib yaseen

# الأفكار المركزية

- 1- connection and parallel CSC.
- 2 – voltage in parallel circuits
- 3 – current in parallel circuits
- 4 – Total Resistance =
- 5- Total Conductance
- 6 – Power
- 7 – CDR
- 8 – Example
- 9 - Homeworks
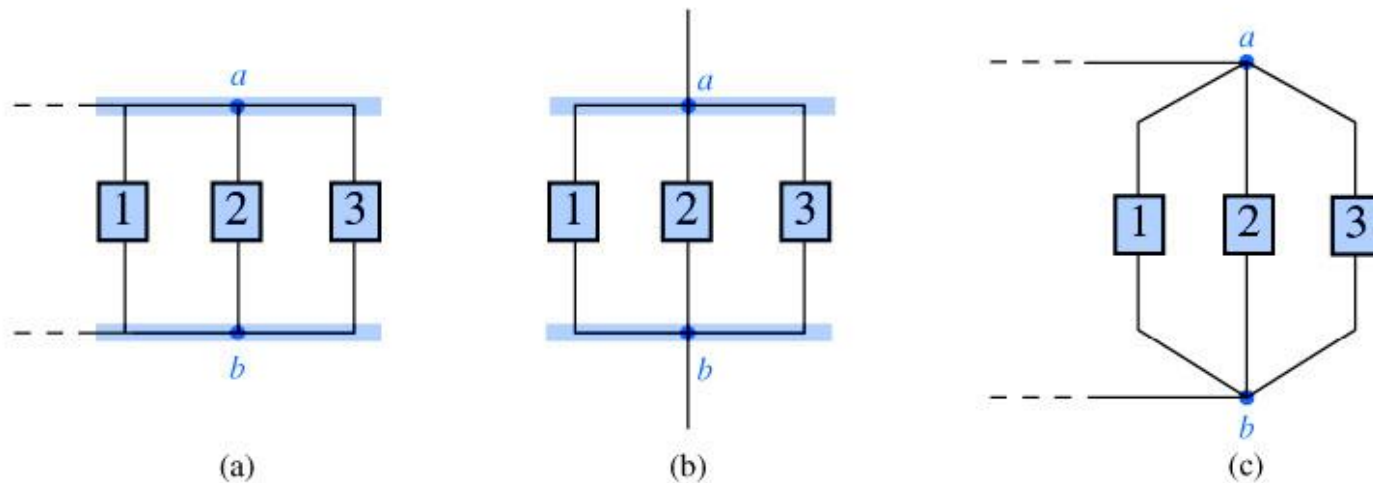
# 1- Parallel Resistors Connection

Two elements, branches, or circuits are in parallel if they have two points in common as in the figure below



## Q- Write the CSC of parallel Resistors

- 1- Same voltage is on all Resistances  $E = V_1 = V_2$
- 2- Current is shared between the Resistances
- 3 – Current in each Resistor is given by ohm ,s Law
- 4- Total Current is equal to the sum of branche Currents

$$I = I_1 + I_2$$

- 5- Total Resistance is given by

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots + \frac{1}{R_N}$$

6- Total Conductance is the sum of parallel conductance

$$G_t = G_1 + G_2$$

$$G = \frac{1}{R}$$


7- For equal Resistors

$$R_T = \frac{R}{N}$$

8- The smaller the Resistance , the greater the current


9- Total power is the sum of powers in each Resistor

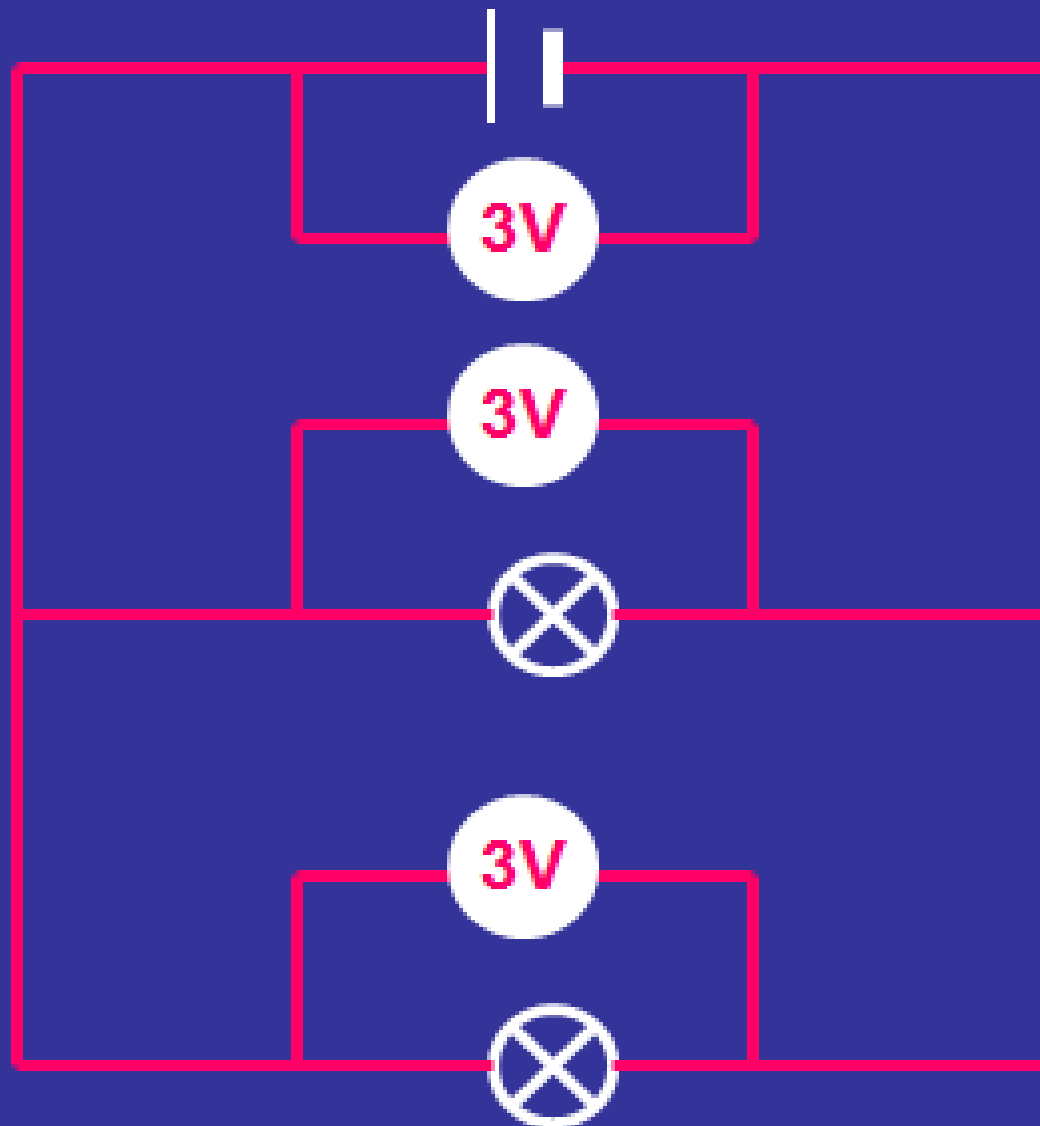voltage is the **same** in all parts of the circuit.


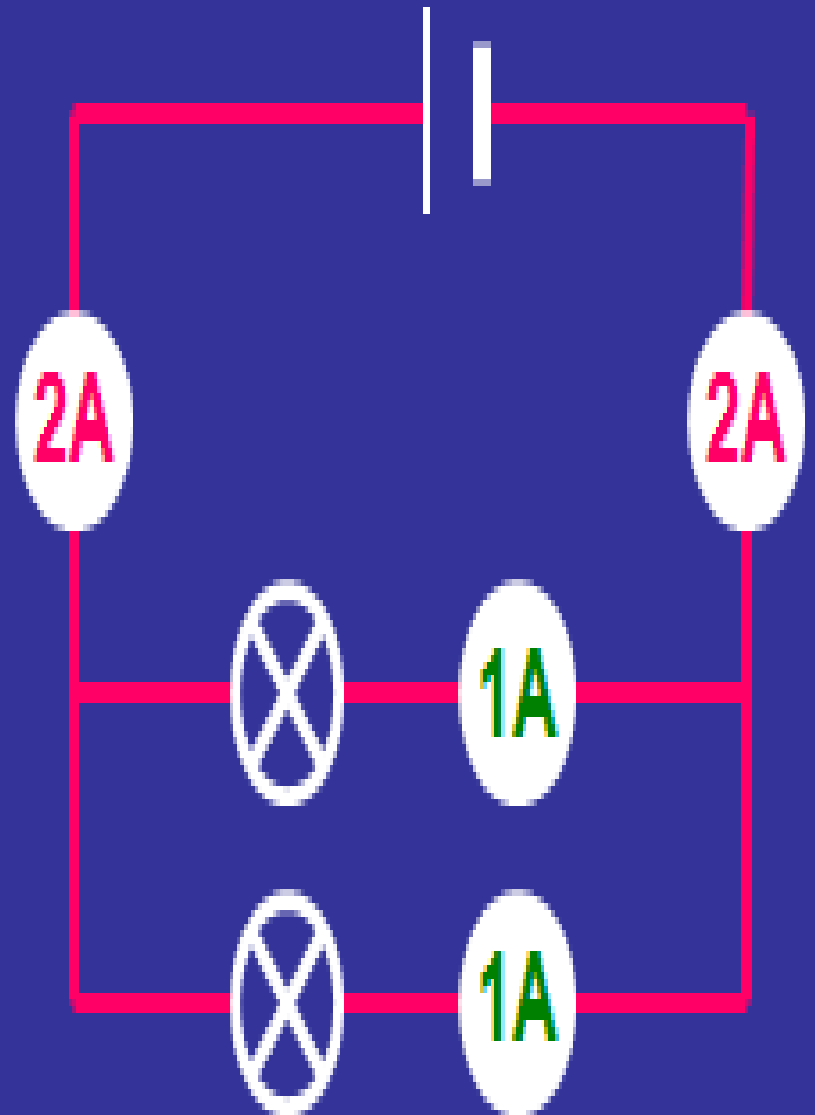
# PARALLEL CIRCUIT

- current is shared between the components



# 3- Total current

- ⌘ For single-source parallel networks, the source current ( $I_s$ ) is equal to the sum of the individual branch currents.

$$I_s = I_1 + I_2$$

- ⌘ For a parallel circuit, source current equals the sum of the branch currents. For a series circuit, the applied voltage equals the sum of the voltage drops.



## 4 – Branch Currents

- ⚡ For parallel circuits, the greatest current will exist in the branch with the lowest resistance.

$$I_s = I_1 + I_2 = \frac{E}{R_1} + \frac{E}{R_2}$$

# 5- Total Parallel Resistors

⚡ For resistors in parallel, the total resistance is determined from

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots + \frac{1}{R_N}$$

# 6 – Total Parallel Resistors Formula

- ⚡ The total resistance of two resistors is the product of the two divided by their sum.

If  $R_1 // R_2$

$$R_T = \frac{R_1 R_2}{R_1 + R_2}$$

If  $R_1 // R_2 // R_3$

$$R_t = \frac{R_1 R_2 R_3}{R_1 R_2 + R_2 R_3 + R_3 R_1}$$

# 7 - Parallel Resistors

♋ For equal resistors in parallel:

$$R_T = \frac{R}{N}$$

Where N = the number of parallel resistors.

# 8 – Total conductance

- ⌘ For parallel elements, the total conductance is the sum of the individual conductance values.

$$G_T = G_1 + G_2 + G_3 + \dots + G_N$$

- ⌘ As the number of resistors in parallel increases, the input current level will increase for the same applied voltage.
- ⌘ This is the opposite effect of increasing the number of resistors in a series circuit.

## 9- Power Distribution in a Parallel Circuit

- ⌘ For any resistive circuit, the power applied by the battery will equal that dissipated by the resistive elements.

$$P_E = P_{R_1} + P_{R_2} + P_{R_3} + \dots + P_{R_N}$$

- ⌘ The power relationship for parallel resistive circuits is identical to that for series resistive circuits.

# 10 - Current Divider Rule

- ⌘ The **current divider rule (CDR)** is used to find the current through a resistor in a parallel circuit.

$$I_x = \frac{R_T}{R_x} I_T$$

- ⌘ General points:

- ⌘ For two parallel elements of equal value, the current will divide equally.
- ⌘ For parallel elements with different values, the smaller the resistance, the greater the share of input current.
- ⌘ For parallel elements of different values, the current will split with a ratio equal to the inverse of their resistor values.

Example : 12 Two Resistances  $3 \Omega$  ,  $6 \Omega$  are connected in parallel to  $12 \text{ V}$  supply , calculate :

- 1- Total Resistance
- 2 – Total current
- 3 – branch current
- 4- total power consumed

Solution :

$$1 - R_t = R_1 // R_2 = \frac{R_1 * R_2}{R_1 + R_2} = \frac{3 * 6}{3 + 6} = 2 \Omega$$

$$2- I_1 = \frac{V}{R_1} = \frac{12}{3} = 4 \text{ A}$$

$$I_2 = \frac{V}{R_2} = \frac{12}{6} = 2 \text{ A}$$

$$3 - I_t = I_1 + I_2 = 4 + 2 = 6 \text{ A}$$

$$\text{OR } I_t = \frac{V}{R_t} = \frac{12}{2} = 6 \text{ A}$$

$$4- P_1 = I_1^2 R_1 = 4^2 * 3 = 16 * 3 = 48 \text{ W}$$

$$P_2 = I_2^2 R_2 = 2^2 * 6 = 4 * 6 = 24 \text{ W}$$

$$P_t = p_1 + p_2 = 48 + 24 = 72 \text{ w}$$

$$\text{Or } P_t = I_t^2 R_t = 6^2 * 2 = 36 * 2 = 72 \text{ w}$$



# Example :13

Two Resistances  $5\Omega$  ,  $20\Omega$  are connected in parallel ,  
use ( CDR ) find the current through each resistor if  
the total current is (  $10\text{ A}$  )

Solution :

$$I_1 = \frac{R_2}{R_1+R_2} I = \frac{20}{5+20} * 10 = \frac{20}{25} * 10 = 8\text{ A}$$


$$I_2 = \frac{R_1}{R_1+R_2} I = \frac{5}{5+20} * 10 = \frac{5}{25} * 10 = 2\text{ A}$$

# Example : 14

For the circuit shown find :

1- supply voltage

2 – ammeter reading

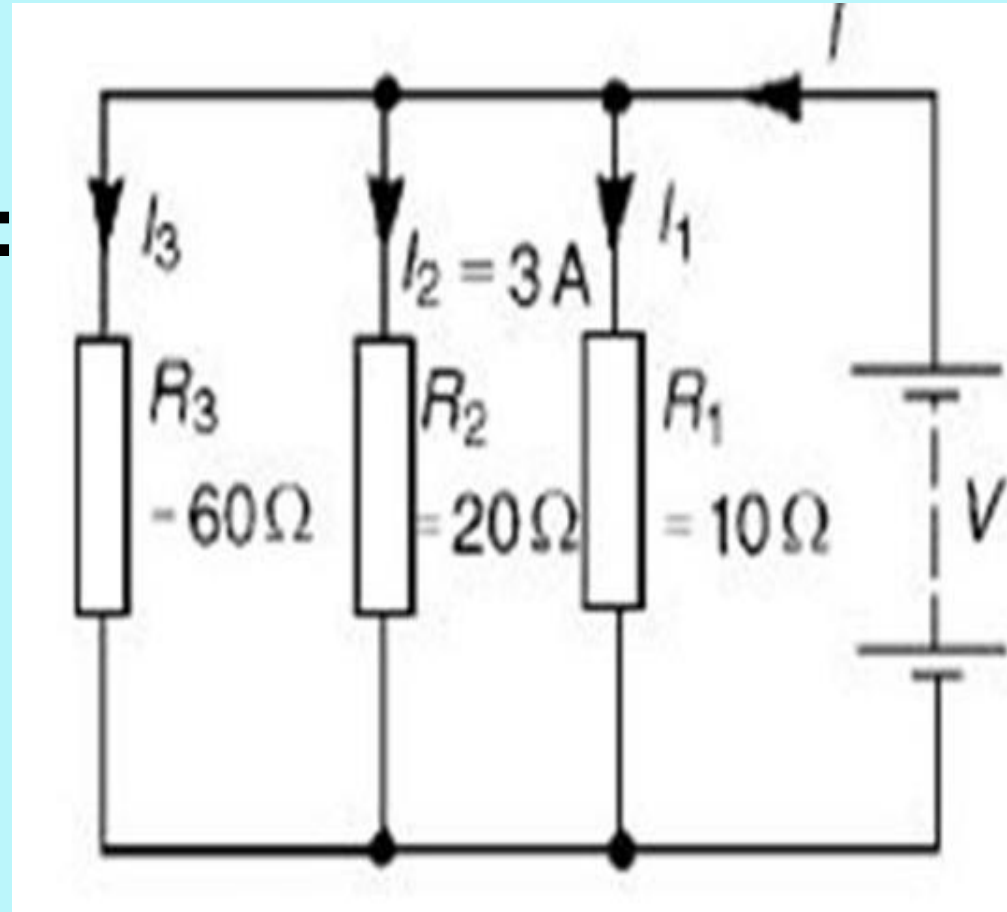

(a) Voltage across  $20\ \Omega$  resistor  $= I_2 R_2 = 3 \times 20 = 60\ \text{V}$ ; hence, supply voltage  $V = 60\ \text{V}$  since the circuit is connected in parallel.

(b) Current  $I_1 = \frac{V}{R_1} = \frac{60}{10} = 6\ \text{A}$ ;  $I_2 = 3\ \text{A}$

$$I_3 = \frac{V}{R_3} = \frac{60}{60} = 1\ \text{A}$$

Current  $I = I_1 + I_2 + I_3$  and hence,  $I = 6 + 3 + 1 = 10\ \text{A}$

Alternatively,  $\frac{1}{R} = \frac{1}{60} + \frac{1}{20} + \frac{1}{10} = \frac{1+3+6}{60} = \frac{10}{60}$


Hence, total resistance  $R = \frac{60}{10} = 6\ \Omega$

Current  $I = \frac{V}{R} = \frac{60}{6} = 10\ \text{A}$
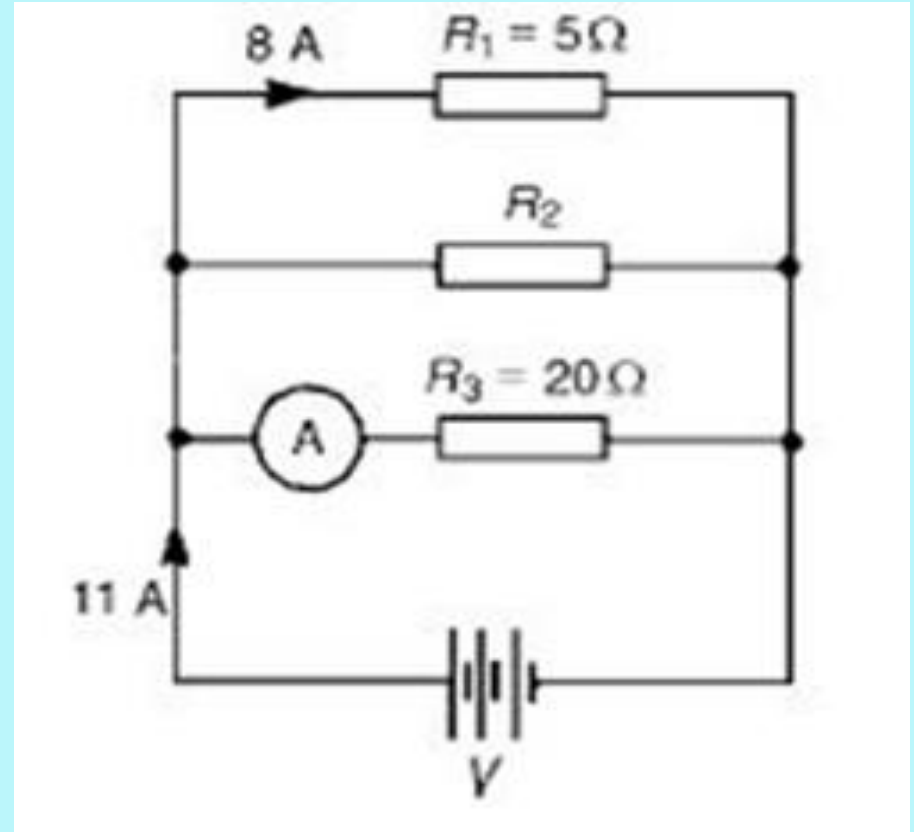
# Example : 15

For the circuit shown find :

- 1- supply voltage
- 2- Total current
- 3 – Branch currents
- 4 – Total Resistance
- 5 – Total power delivered
- 6 – Total power consumed



### ***Solution***

Voltage across  $R_1$  is the same as the supply voltage  $V$ . Hence, supply voltage  $V = 8 \times 5 = 40 \text{ V}$ .


(a) Reading on ammeter,  $I = \frac{V}{R_3} = \frac{40}{20} = 2 \text{ A}$

(b) Current flowing through  $R_2 = 11 - 8 - 2 = 1 \text{ A}$


Hence,  $R_2 = \frac{V}{I_2} = \frac{40}{1} = 40 \Omega$

# Example; 16 - find $R_T$ & $G_T$

**H.W**

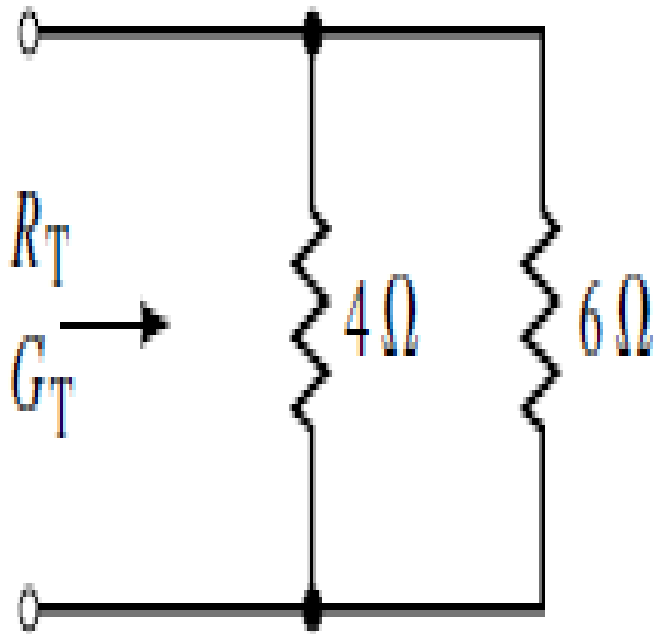


(a)

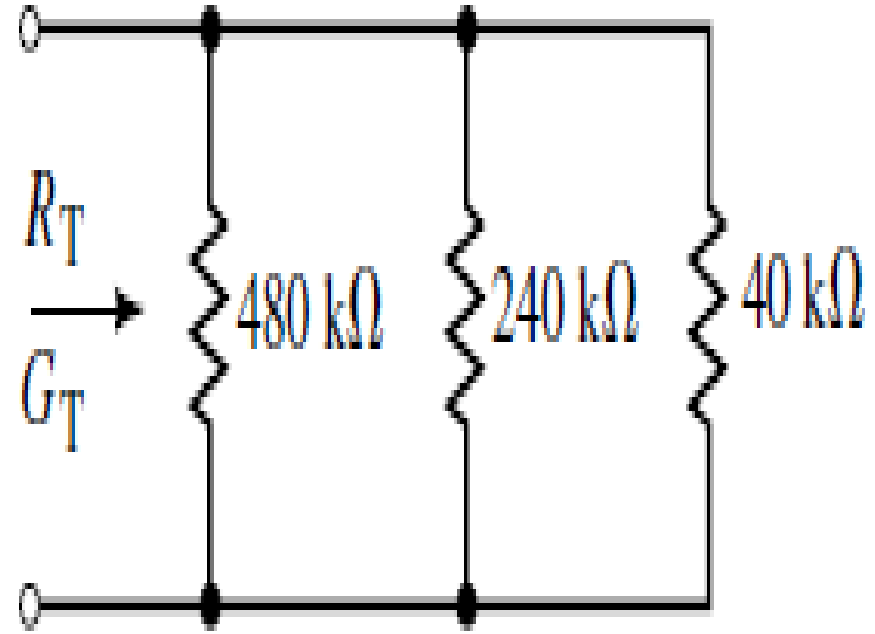


(b)

# Example; 17 - find the value of R

H.W

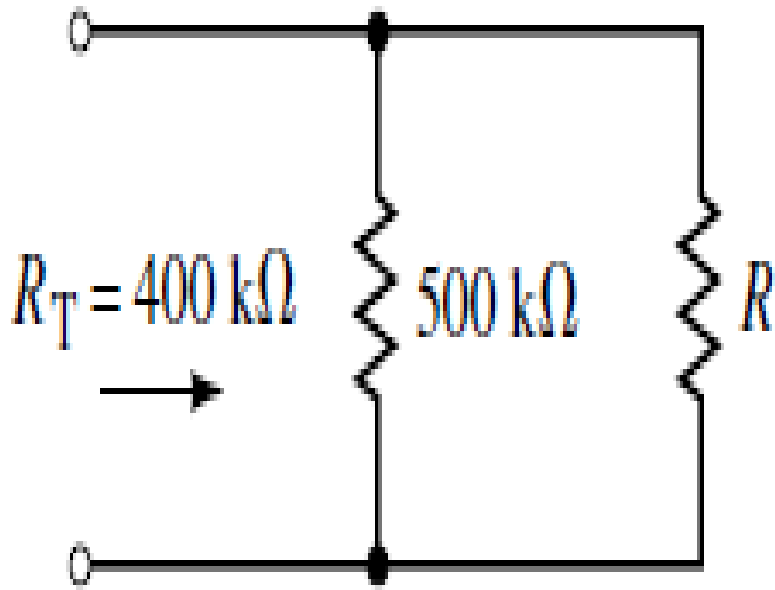


(a)

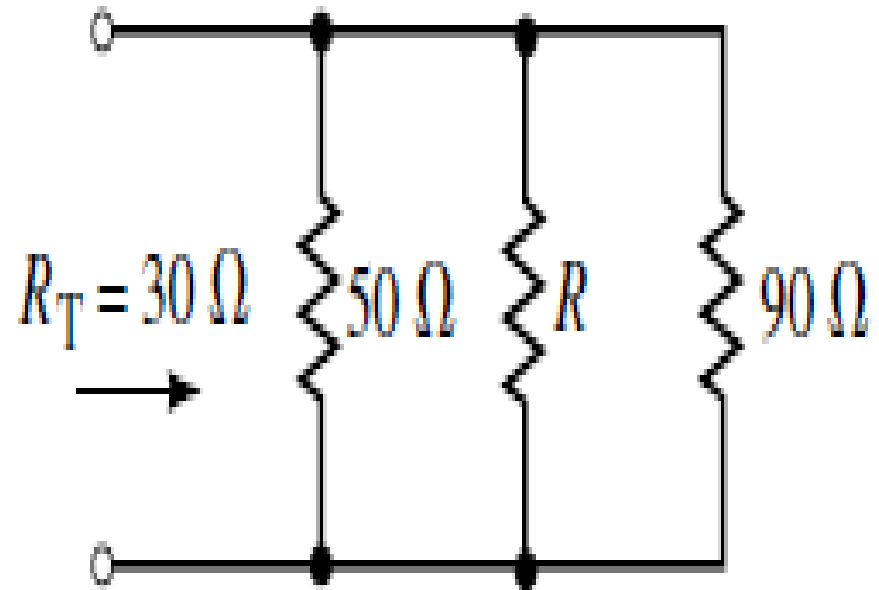

(b)


# Example : 18- Find the indicated current

**H.W**

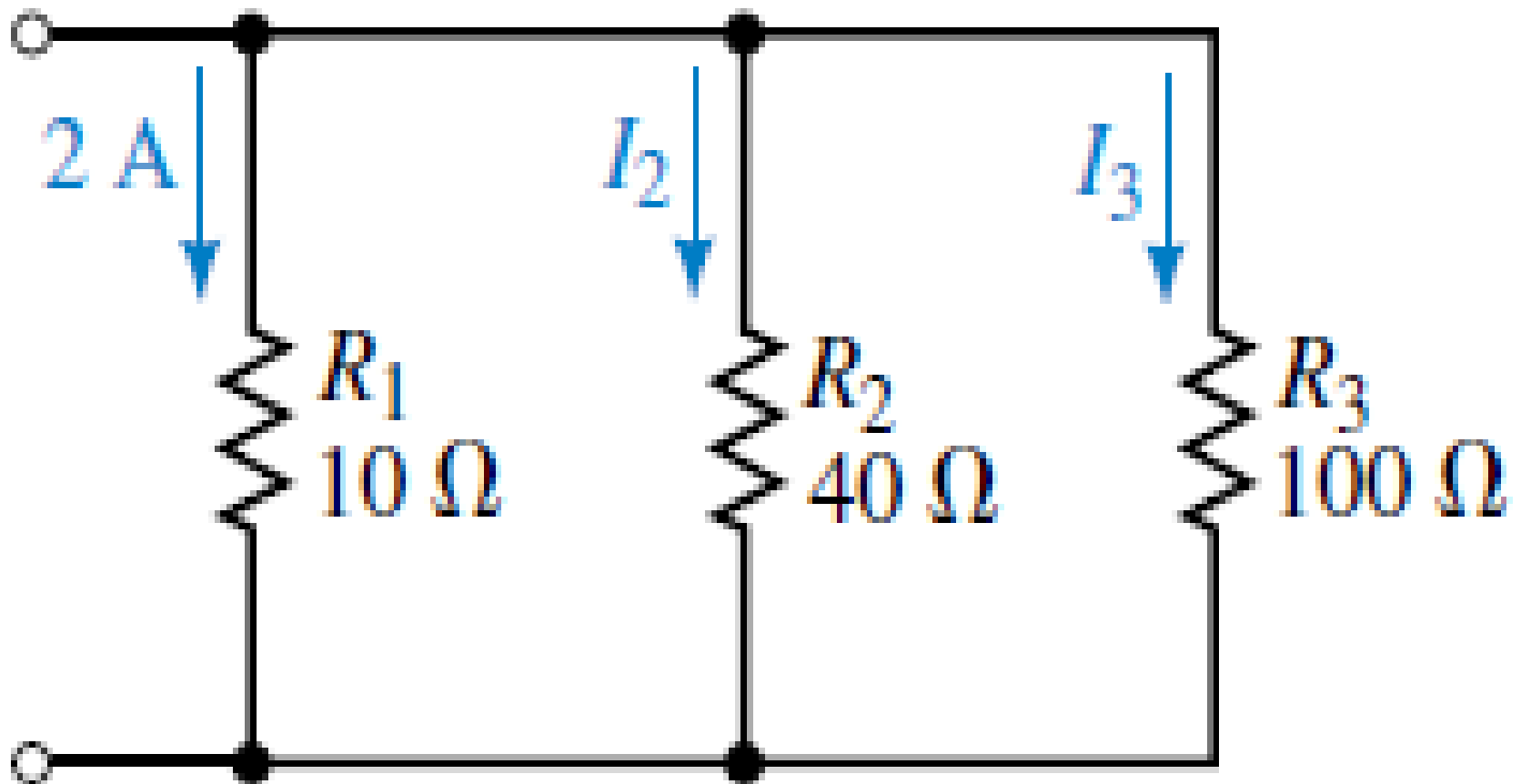



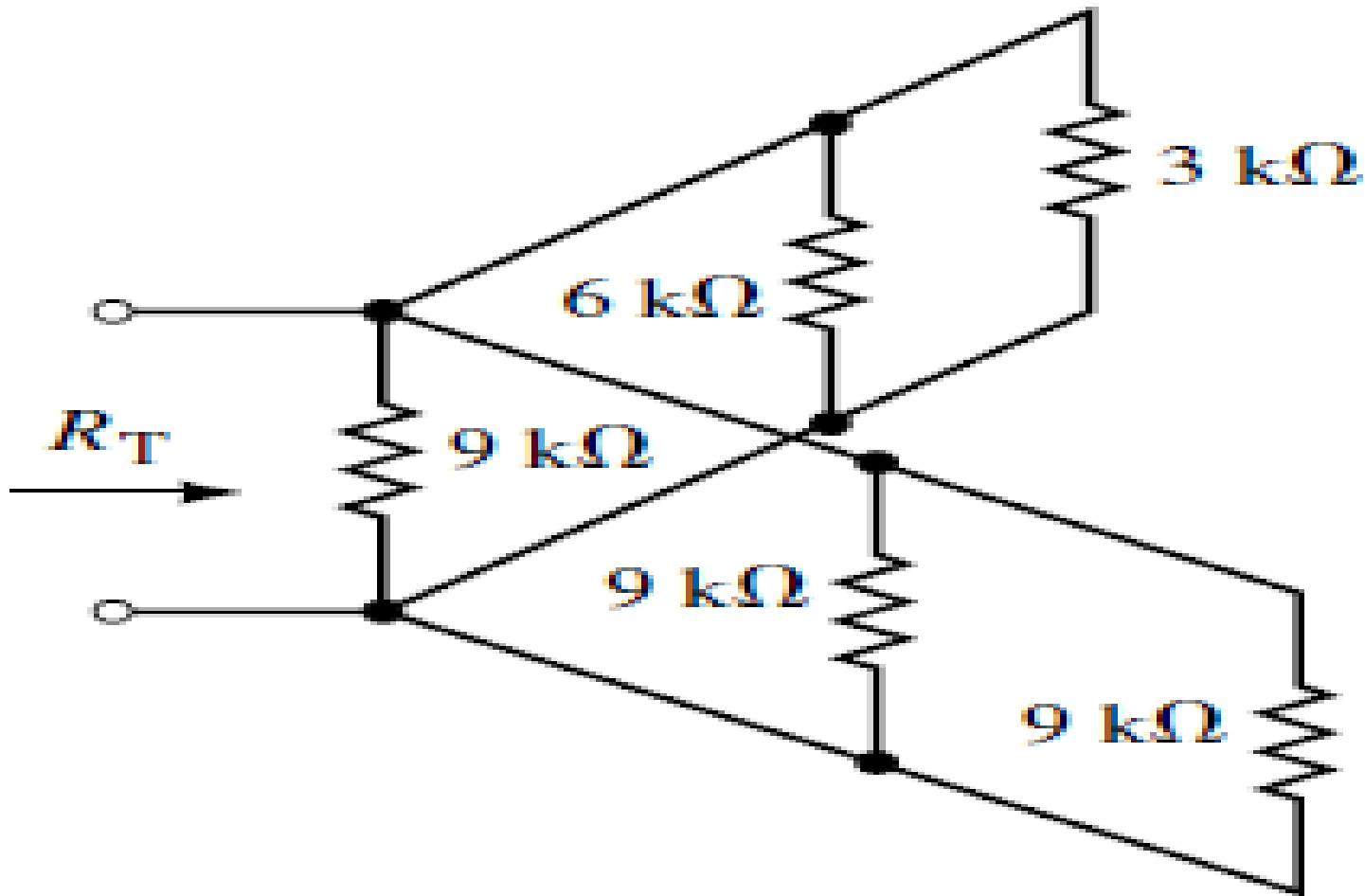
# Example: 19- find the total Resistance ( $R_T$ ) **H.W**


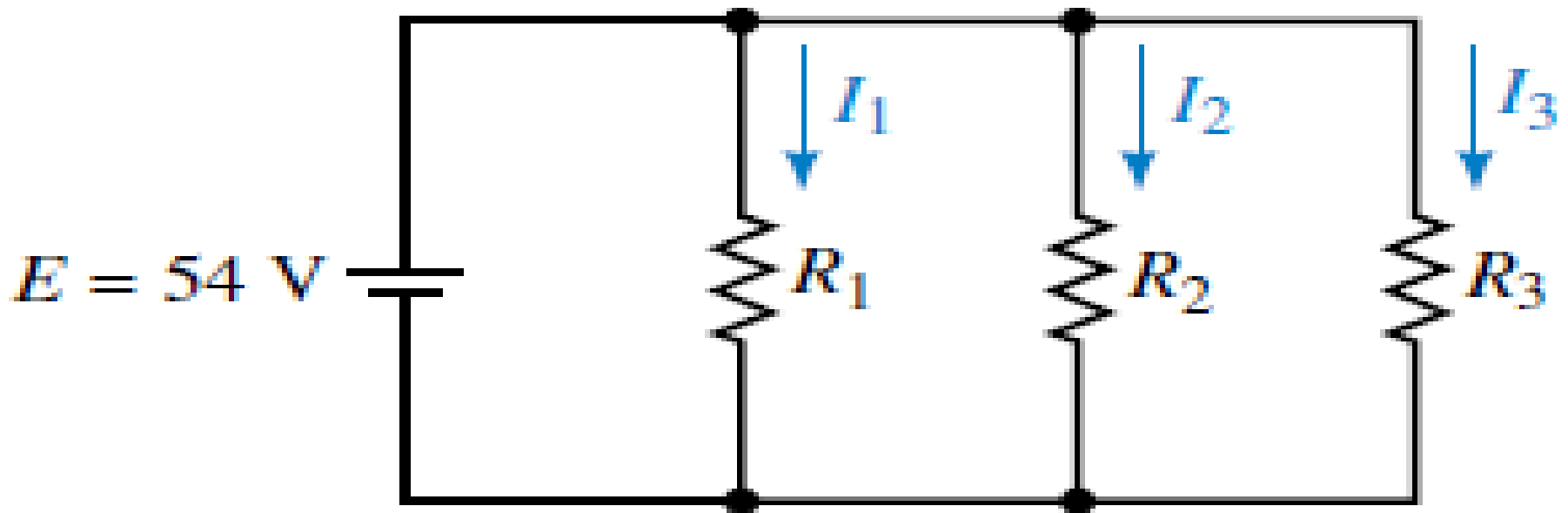
# Example: 20 – find indicated currents and unknown Resistances **H.W**




$$R_1 = 36 \Omega$$

$$I_3 = 500 \text{ mA}$$


$$R_2 = 4R_1$$

# Example: 21 – find $R_T$

**H.W**

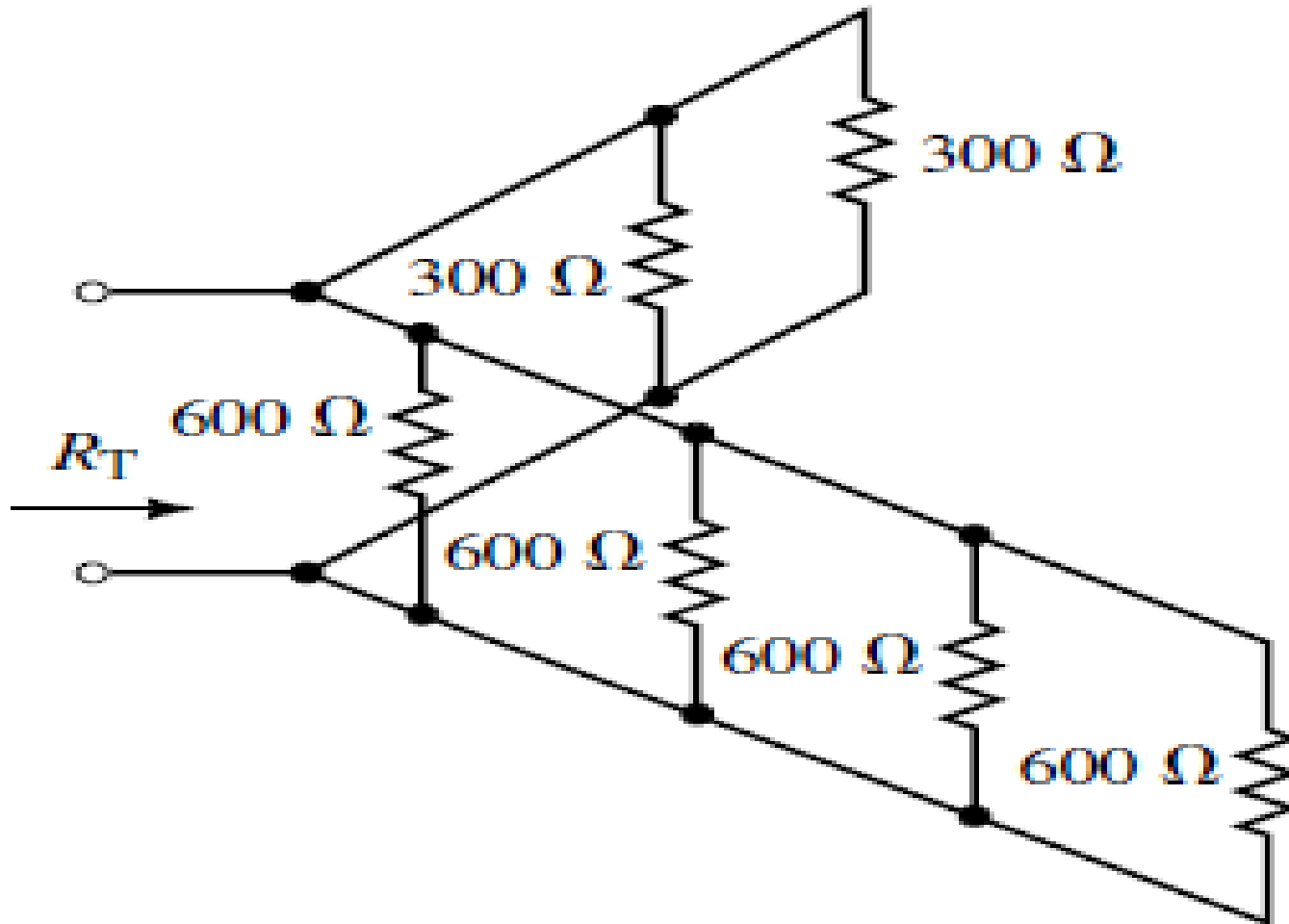

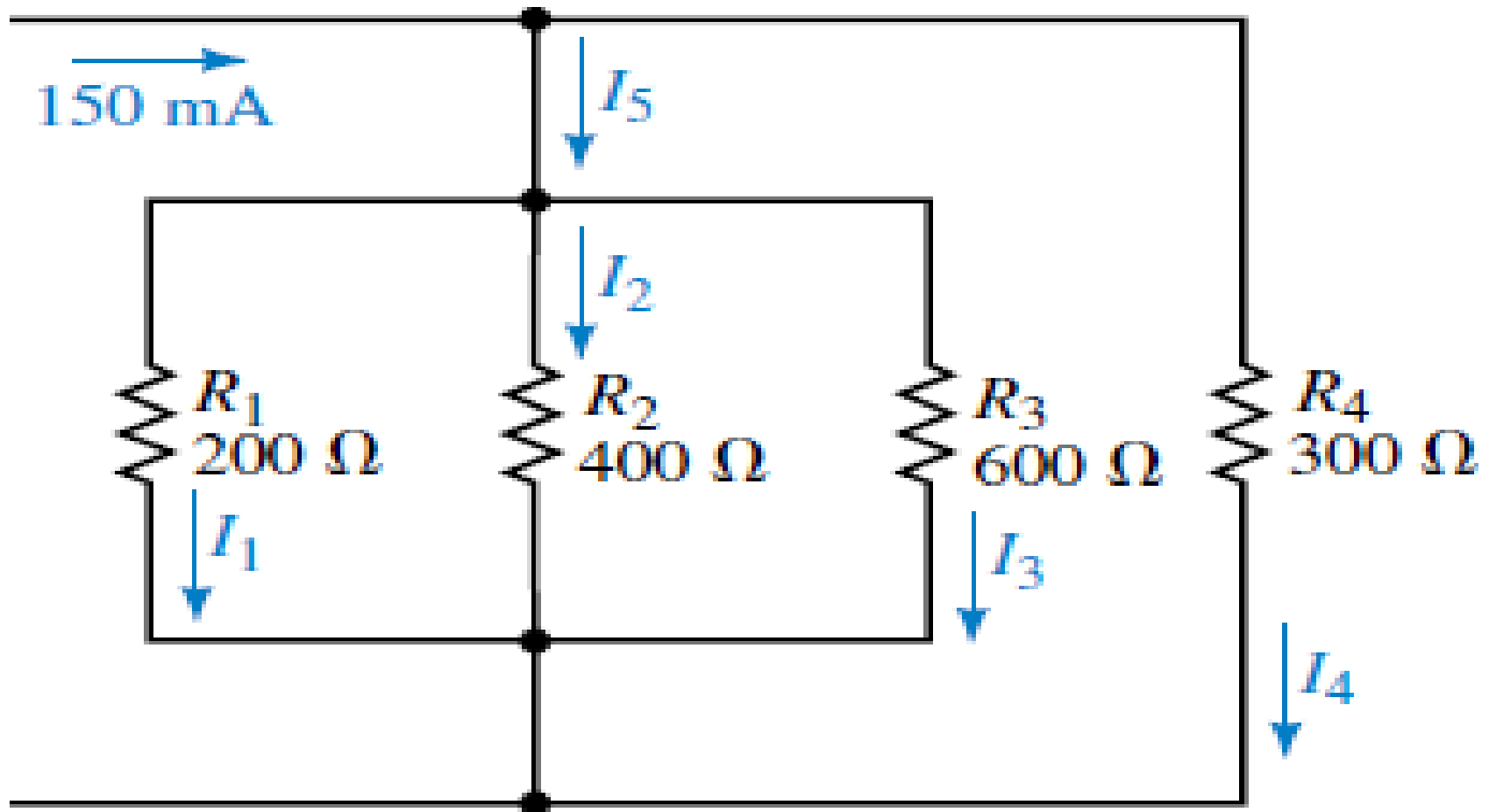
# Example: 22- find the indicated currents **H.W**




# Example: 23- find the indicated currents


**H.W**

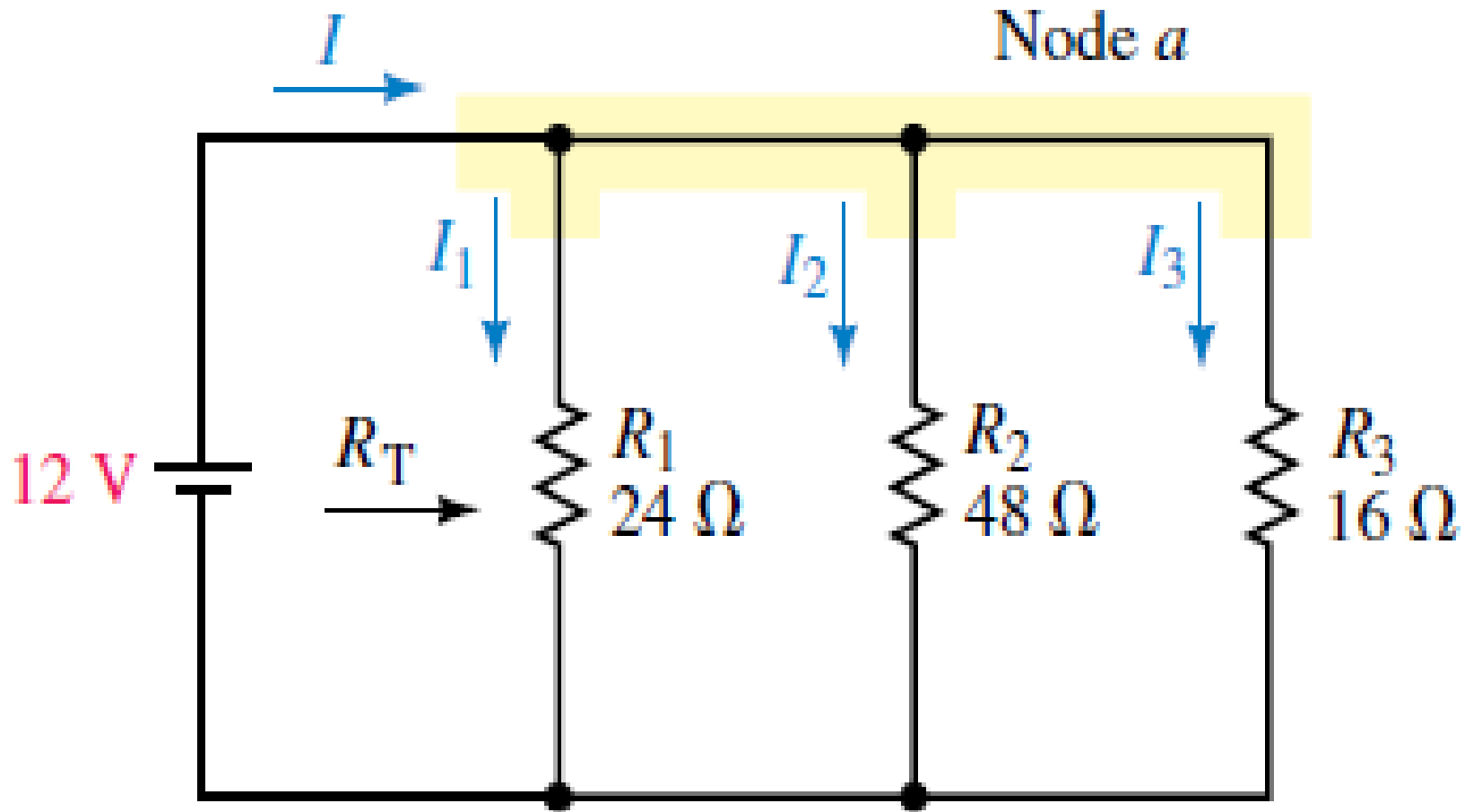

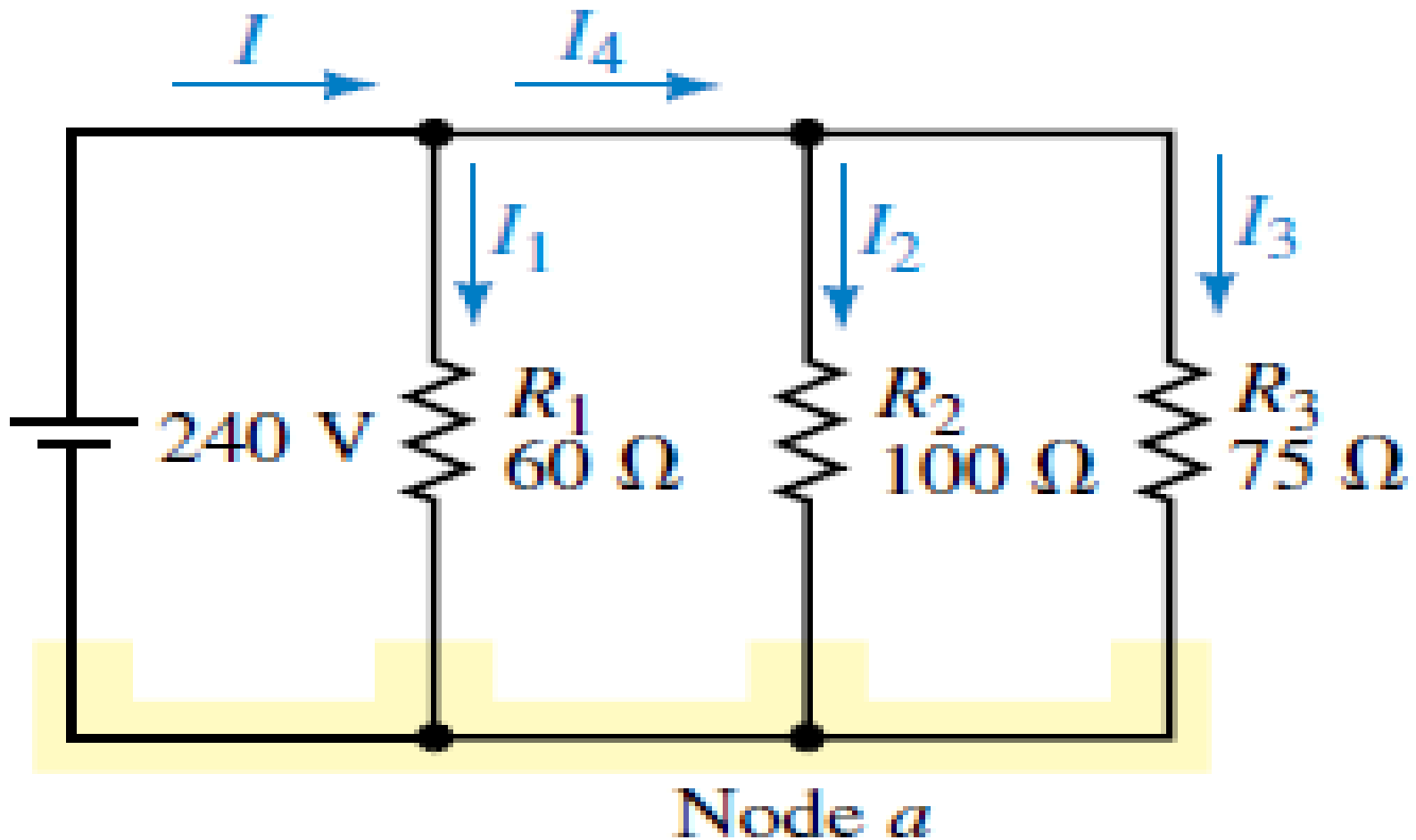
# example: 24- find the indicated currents (H.W)


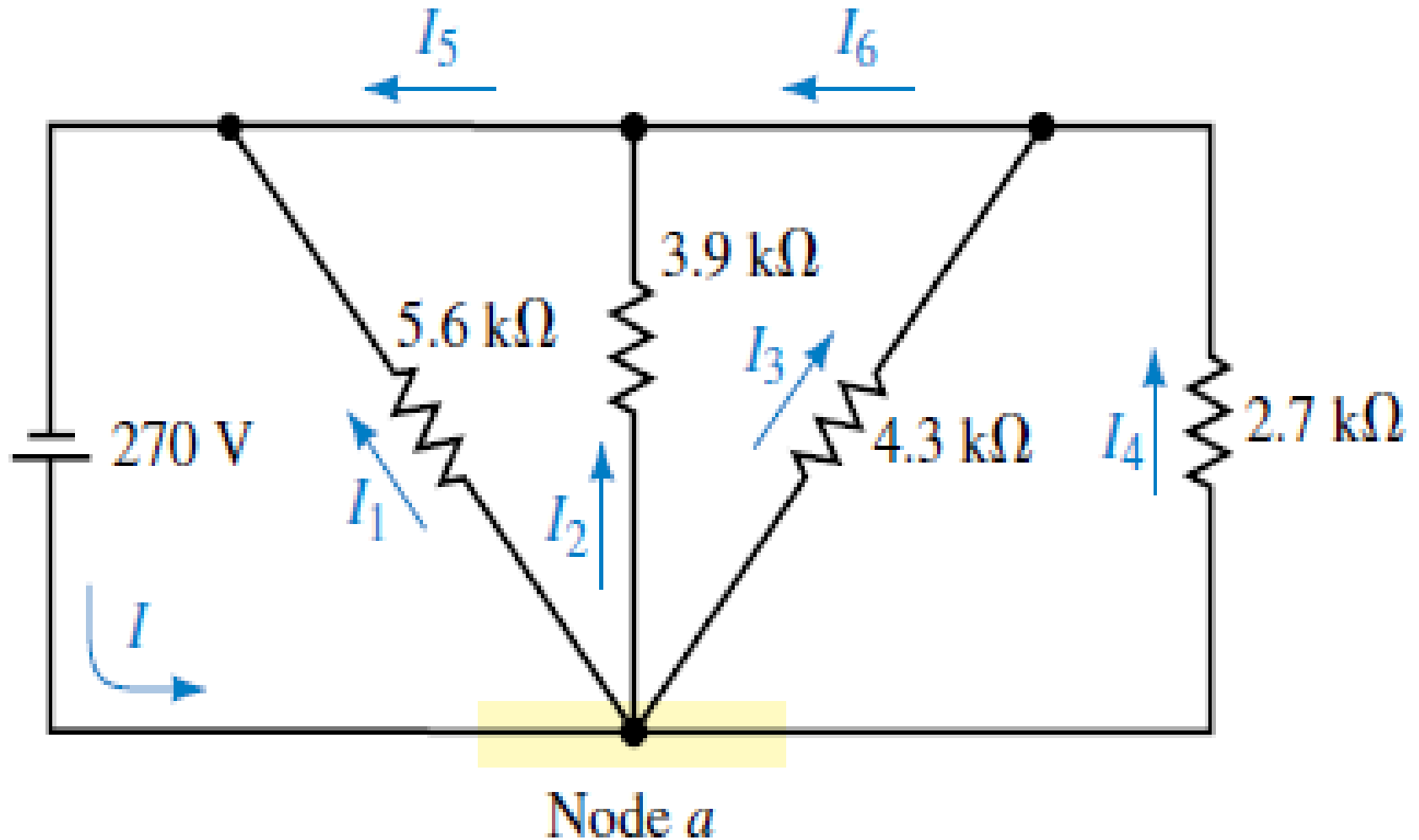
# Example ;25 – find the indicated currents ( H.W )



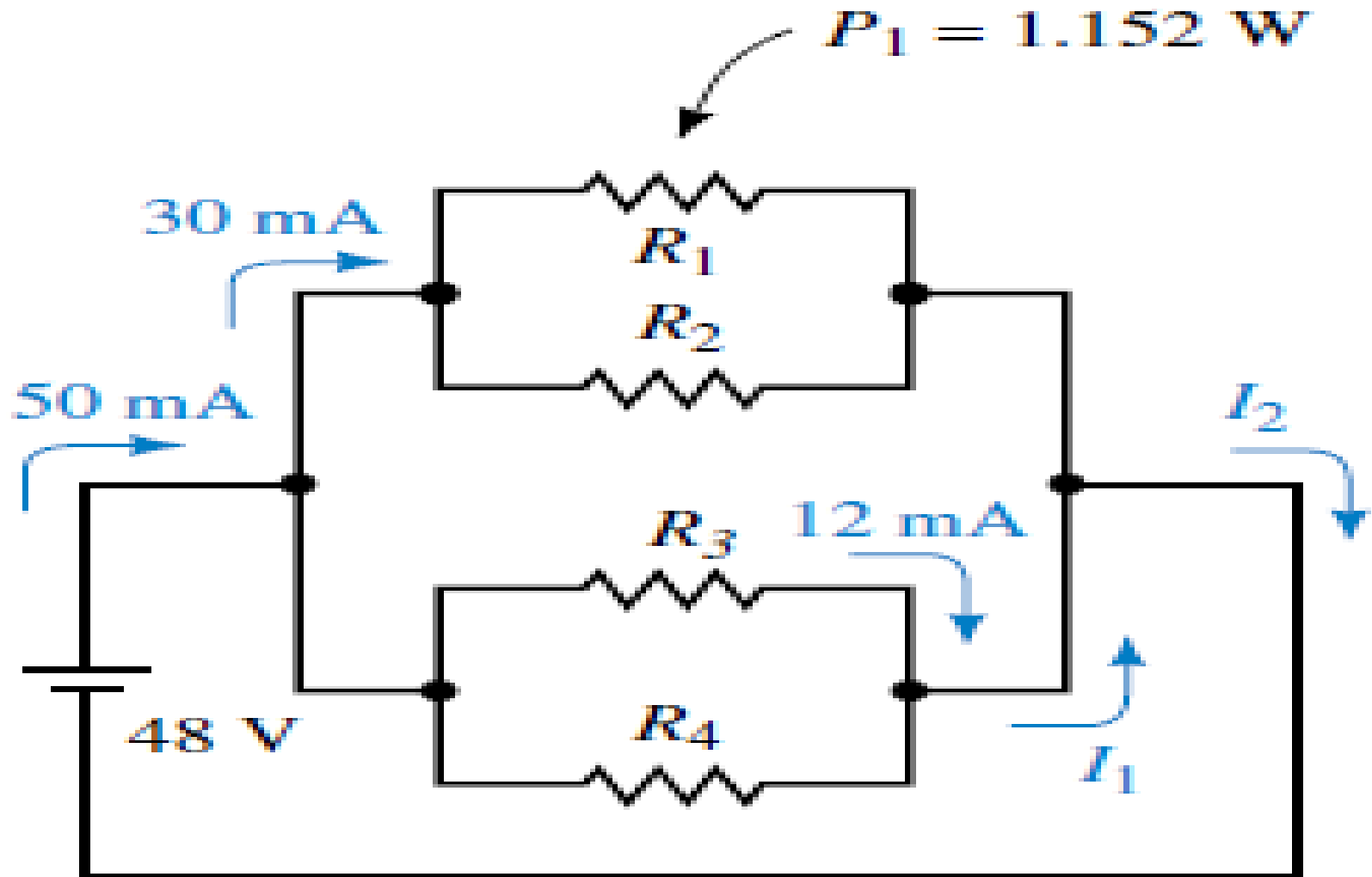
# Example: 26 - find the unknown current and Resistances (H.W)





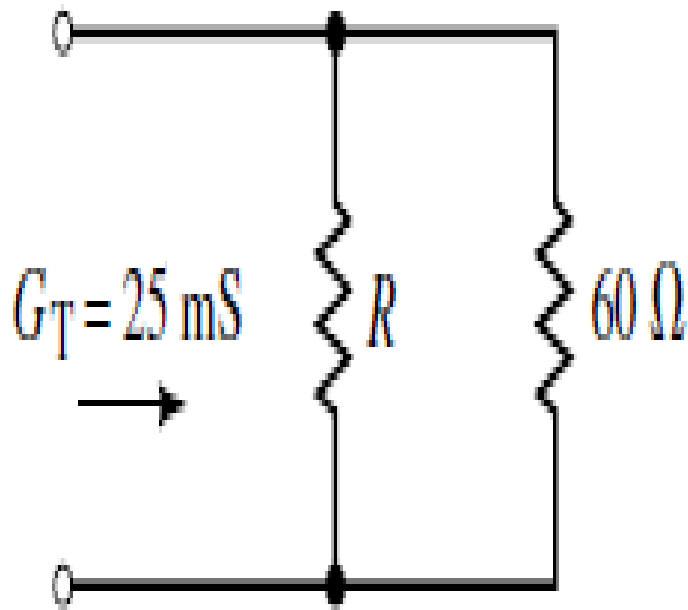
# Example: 27- find the unknown Resistance **H.W**



(a)

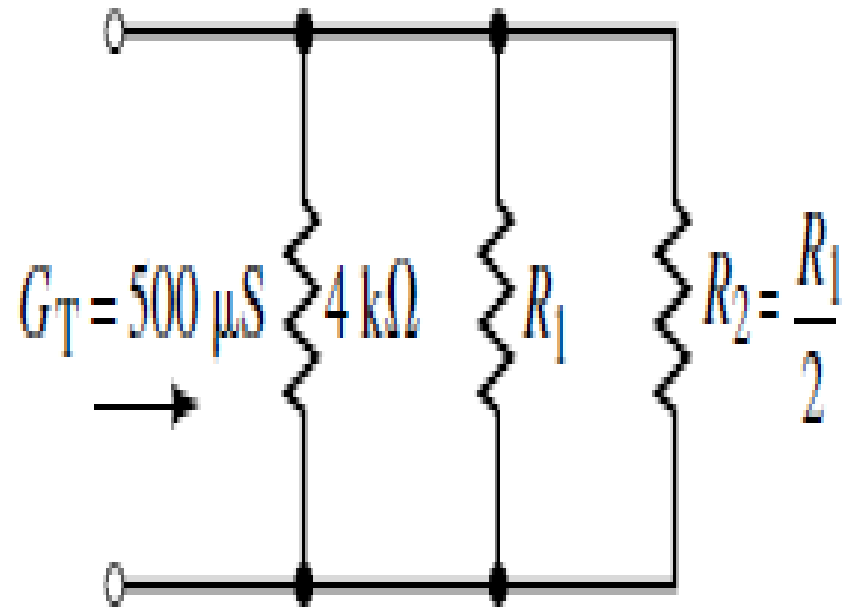

(b)