

## Boolean Algebra and Simplification Techniques

### DeMorgan's Theorem

$$\begin{aligned} (\overline{x + y}) &= \overline{x} \cdot \overline{y} \\ (\overline{x \cdot y}) &= \overline{x} + \overline{y} \end{aligned}$$

Example 1:- let's apply them to the expression  $(\overline{AB} + C)$  as shown below:

$$(\overline{AB} + C) = (\overline{AB}) \cdot \overline{C}$$

$$\overline{AB} \cdot \overline{C} = (\overline{A} + \overline{B}) \cdot \overline{C}$$

$$(\overline{A} + B) \cdot \overline{C} = \overline{A}\overline{C} + B\overline{C}$$

### Example 2:-

Simplify the expression  $z = \overline{(\overline{A} + C) \cdot (B + \overline{D})}$  to one having only single variables inverted.

#### **Solution**

$$\begin{aligned} z &= (\overline{\overline{A} + C}) + (\overline{B + \overline{D}}) \\ z &= (\overline{\overline{A} + C}) + (\overline{B} \cdot \overline{\overline{D}}) \\ &= (\overline{\overline{A} \cdot \overline{C}}) + \overline{B} \cdot \overline{\overline{D}} \\ z &= A\overline{C} + \overline{B}D \end{aligned}$$

### **H.W.**

$$z = \overline{A + \overline{B} \cdot C}$$

$$\omega = \overline{(A + BC) \cdot (D + EF)}$$

**Rules of Boolean Algebra:-**

1.  $A + 0 = A$

7.  $A \cdot A = A$

2.  $A + 1 = 1$

8.  $A \cdot \bar{A} = 0$

3.  $A \cdot 0 = 0$

9.  $\bar{\bar{A}} = A$

4.  $A \cdot 1 = A$

10.  $A + AB = A$

5.  $A + A = A$

11.  $A + \bar{A}B = A + B$

6.  $A + \bar{A} = 1$

12.  $(A + B)(A + C) = A + BC$

**Example 1:** Using Boolean Algebra techniques, simplify the following expression:

1 -  $X(\bar{X} + Y)$


2 -  $AB(C + \bar{A}\bar{C})$

3 -  $ABC + A\bar{B}C + A\bar{B}\bar{C}$


Solution:-

$$\begin{aligned} 1 - X(\bar{X} + Y) \\ = X\bar{X} + XY \\ = XY \end{aligned}$$
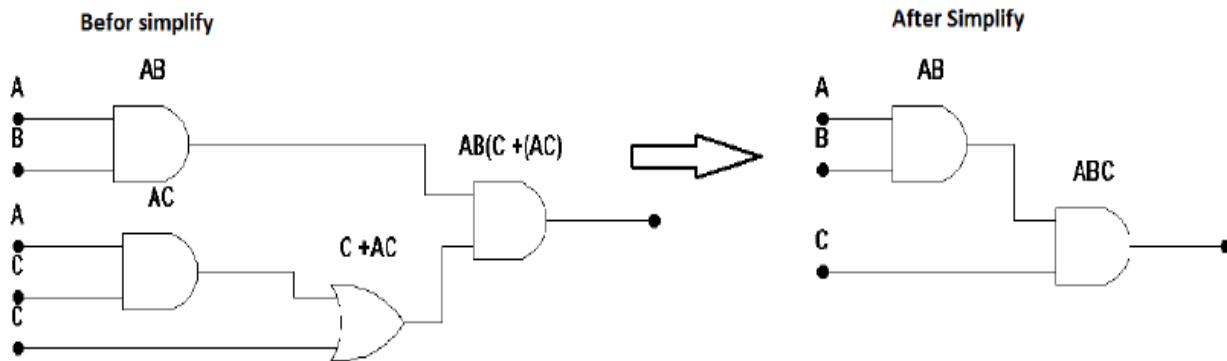
$$\begin{aligned} 2 - AB(C + \bar{A}\bar{C}) \\ = ABC + A\bar{B}\bar{A}\bar{C} \\ = ABC + (A\bar{A})B\bar{C} \\ = ABC + 0 \cdot B\bar{C} \\ = ABC + 0 \\ = ABC \end{aligned}$$


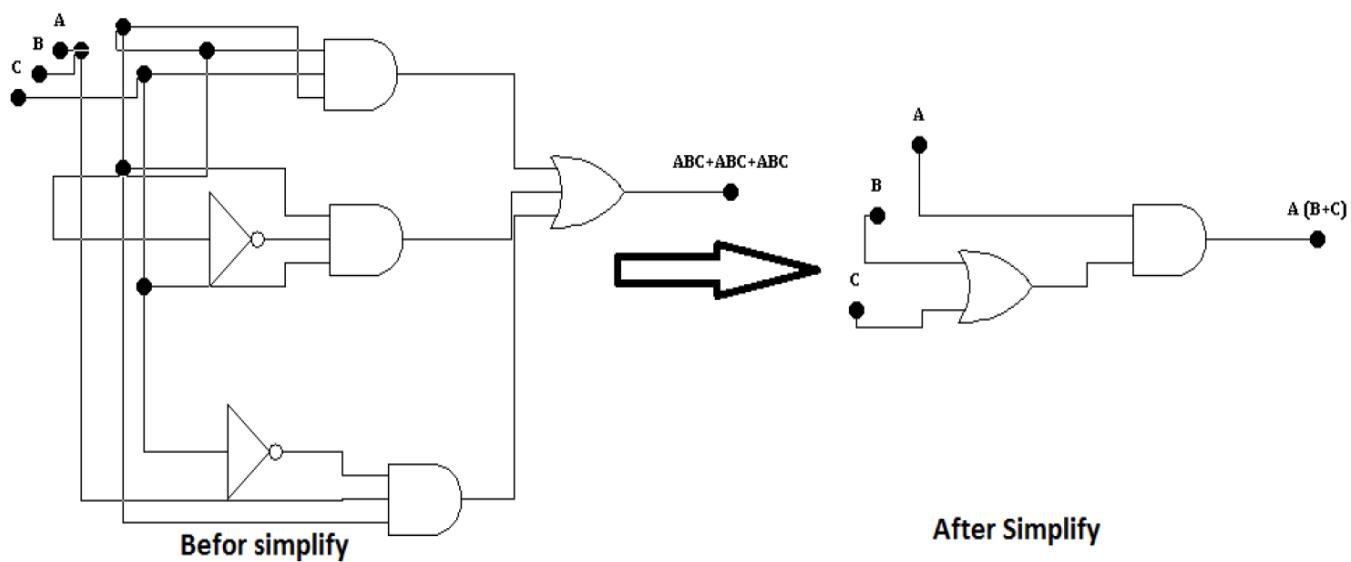
$$\begin{aligned}
 3 - ABC + A\bar{B}C + A\bar{B}\bar{C} \\
 &= AC(B + \bar{B}) + A\bar{B}\bar{C} \\
 &= AC \cdot 1 + A\bar{B}\bar{C} \\
 &= AC + A\bar{B}\bar{C} \\
 &= A(C + \bar{B}\bar{C}) \\
 &= A(C + B)
 \end{aligned}$$



**H.W.**

**1 - Simplify the following expression and Draw the logic circuit before and after simplification**

$$a) A\bar{B} + A(\overline{A+C}) + B(\overline{B+C})$$



$$b) \overline{A}BC + A\overline{B}\overline{C} + \overline{A}\overline{B}\overline{C} + A\overline{B}C + ABC$$

## Arithmetic Circuits

### Half-Adder

$$\text{SUM } S = A \cdot \bar{B} + \bar{A} \cdot B$$

$$\text{CARRY } C = A \cdot B$$

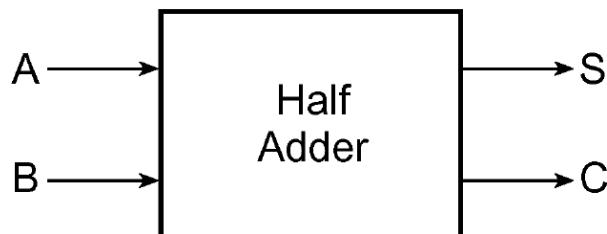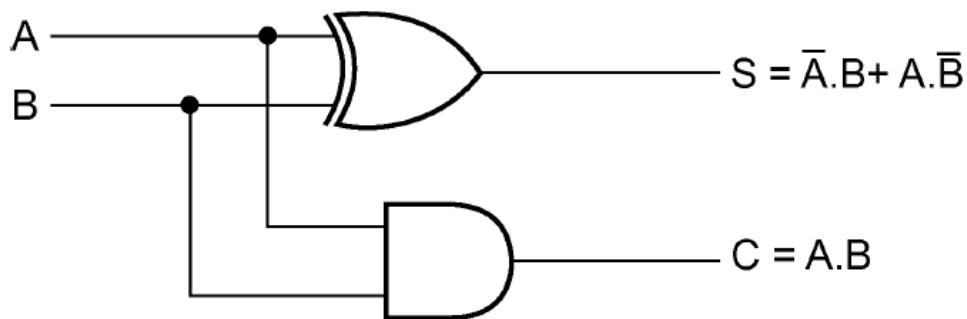

A	B	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

Truth table of a half-adder


## Half-Subtractor

$$D = \overline{A} \cdot B + A \cdot \overline{B}$$

$$B_0 = \overline{A} \cdot B$$


**B<sub>0</sub> = Borrow**

**D=Difference**

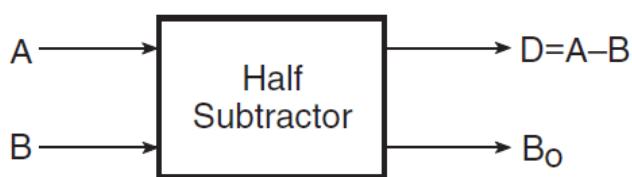

A	B	D	B <sub>0</sub>
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

Logic diagram of a half-subtractor

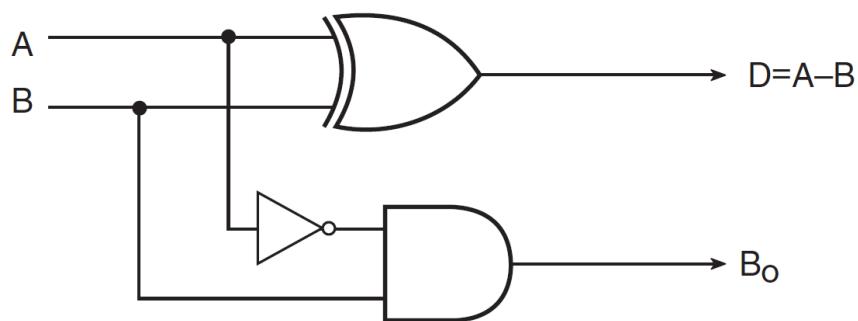

Logic diagram of a half-subtractor