

Karnaugh Map Method

Example 1: Simplify $F = \sum(1,3,7,5)$ by using karnuagh maps

$$\begin{aligned}
 F &= \overline{A}\overline{B}C + \overline{A}BC + ABC + A\overline{B}C \\
 &= \overline{A}C(\overline{B} + B) + AC(B + \overline{B}) \\
 &= \overline{A}C + AC \\
 &= C(\overline{A} + A) = C
 \end{aligned}$$

| | \bar{C} | C |
|------------------|-----------|-----|
| $\bar{A}\bar{B}$ | 0 | 1 |
| $\bar{A}B$ | 0 | 1 |
| $A\bar{B}$ | 0 | 1 |
| AB | 0 | 1 |
| $A\bar{B}$ | 0 | 1 |

$X = C$

Example 2: Simplify $F = \sum(3,2,8,10)$ by using karnuagh maps


Solution

$$\begin{aligned}
 F &= \overline{A}\overline{B}CD + \overline{A}\overline{B}C\overline{D} + A\overline{B}\overline{C}\overline{D} + A\overline{B}CD \\
 &= \overline{A}\overline{B}C + A\overline{B}D
 \end{aligned}$$

| | $\bar{C}\bar{D}$ | $\bar{C}D$ | CD | $C\bar{D}$ |
|------------------|------------------|------------|------|------------|
| $\bar{A}\bar{B}$ | 0 | 0 | 1 | 1 |
| $\bar{A}B$ | 0 | 0 | 0 | 0 |
| $A\bar{B}$ | 0 | 0 | 0 | 0 |
| AB | 1 | 0 | 0 | 1 |

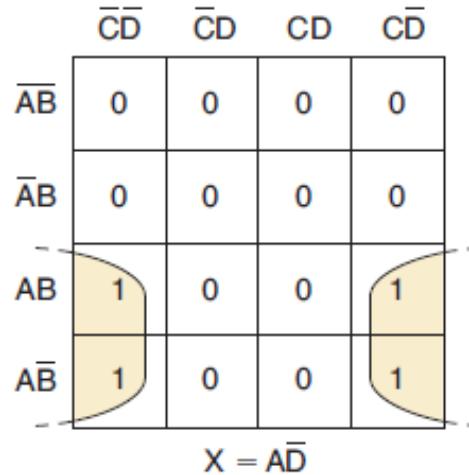Example 3: Simplify $F = \sum(12, 8, 14, 10)$ by using Karnuagh maps

$A\bar{C}\bar{D}$, $A\bar{B}\bar{C}\bar{D}$, $ABC\bar{D}$, and $A\bar{B}C\bar{D}$.




H.W

1- Simplify $F = \sum(12, 13, 15, 14)$ by using karnuagh maps.


R-S Flip-Flop

R-S Flip-Flop with Active High Inputs

| Operation Mode | S | R | Q_{n+1} |
|----------------|---|---|-----------|
| No change | 0 | 0 | Q_n |
| SET | 1 | 0 | 1 |
| RESET | 0 | 1 | 0 |
| Forbidden | 1 | 1 | — |

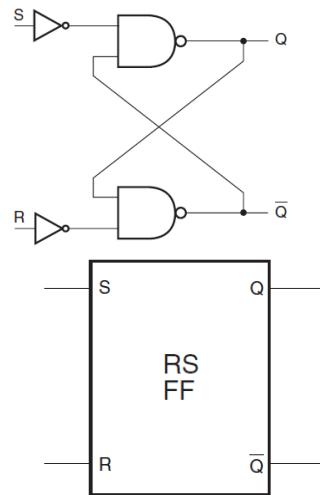

J-K Flip Flop

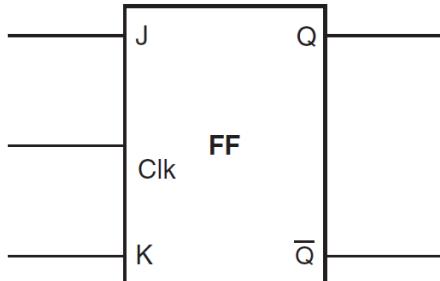

| Operation Mode | J | K | Clk | Q_{n+1} |
|----------------|---|---|-----|-------------|
| SET | 1 | 0 | 1 | 1 |
| RESET | 0 | 1 | 1 | 0 |
| NO CHANGE | 0 | 0 | 1 | Q_n |
| TOGGLE | 1 | 1 | 1 | \bar{Q}_n |

J-K flip-flop active High inputs.

- 1- J-K in Flip Flop
- 2- J-K close similar to R-S
- 3- J-K لا يوجد بها (نوت فالد) (Note: There is no)