

Experiment. N (2)

EX. Name : (Operate a set of loads from two places)

Objective:


The student will be able to :

*Connect circuit to control Operating a set of loads from two places.

*Drawing main and power circuits.

*Convert the ladder diagram to function block diagram and running both circuit in PC and manually.


The main circuit

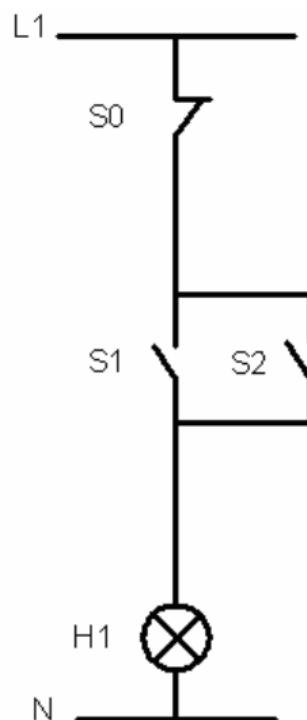

Addressing box

S ₀	I _{0.0}
S ₁	I _{0.1}
S ₂	I _{0.2}
H ₁	Q _{0.0}

Ladder Diagram

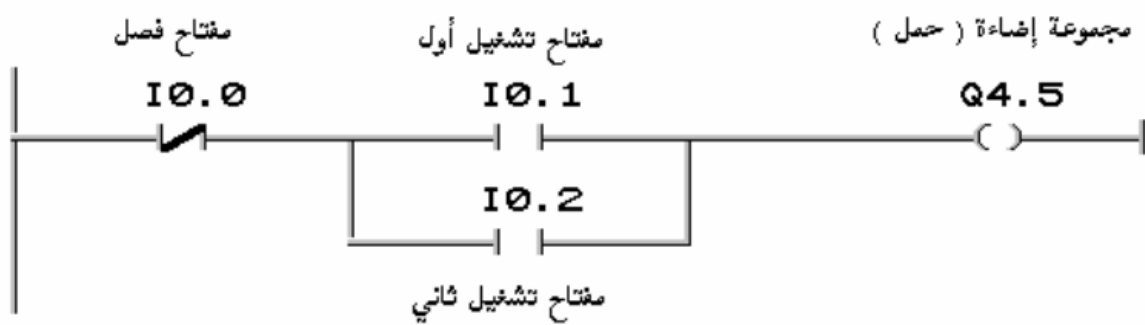

المخطط السلمي

Discussion:

- 1- Draw the circle using FBD.
- 2- Draw the circle to operate lamp from three place using ladder diagram .