

Serial-Parallel Circuits

Introduction

- ⌘ A series-parallel configuration is one that is formed by a combination of series and parallel elements.
- ⌘ A complex configuration is one in which none of the elements are in series or parallel.

Reduce and Return Approach

⌘ Reduce:

⌘ Reduce the circuit to its simplest form across the source and then determine the source current (I_s).

⌘ Return:

⌘ Using the resulting source current (I_s) to work back to the desired unknown.

Problem 11. Resistances of $10\ \Omega$, $20\ \Omega$ and $30\ \Omega$ are connected (a) in series and (b) in parallel to a $240\ \text{V}$ supply. Calculate the supply current in each case.

(a) The series circuit is shown in Fig. 5.21

The equivalent resistance

$$R_T = 10\ \Omega + 20\ \Omega + 30\ \Omega = 60\ \Omega$$

$$\text{Supply current } I = \frac{V}{R_T} = \frac{240}{60} = 4\ \text{A}$$

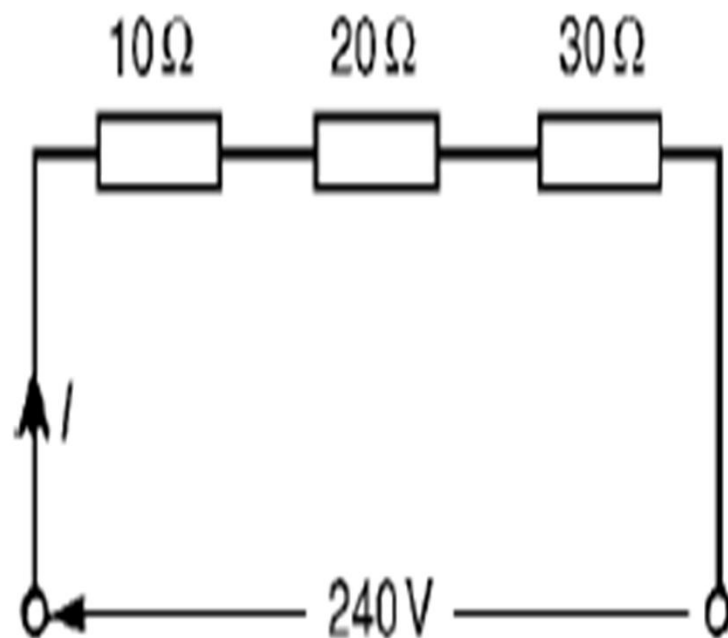


Figure 5.21

B – When the Resistances are connected in parallel

$$\frac{1}{R_T} = \frac{1}{10} + \frac{1}{20} + \frac{1}{30} = \frac{6 + 3 + 2}{60} = \frac{11}{60}$$

$$\text{hence } R_T = \frac{60}{11} \Omega$$

Supply current

$$I = \frac{V}{R_T} = \frac{240}{\frac{60}{11}} = \frac{240 \times 11}{60} = 44 \text{ A}$$

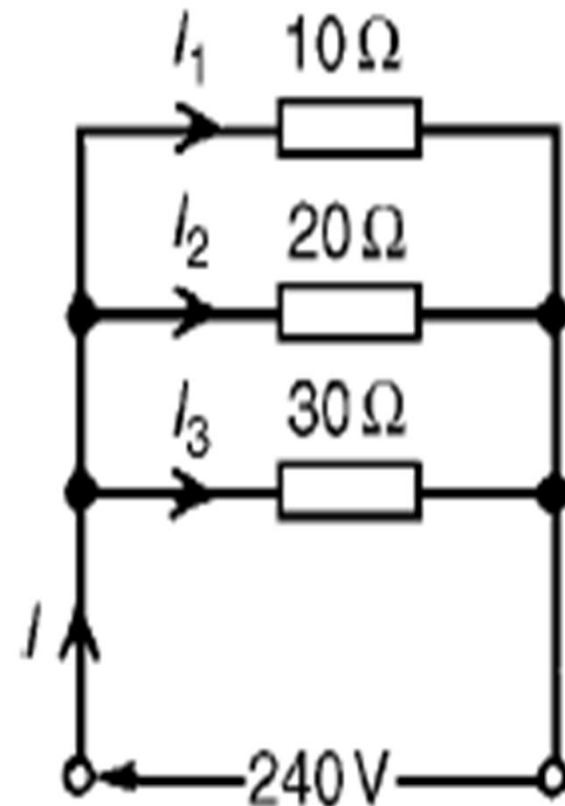


Figure 5.22

Problem 12. For the series-parallel arrangement shown in Fig. 5.24, find (a) the supply current, (b) the current flowing through each resistor and (c) the p.d. across each resistor.

p.d. : potential difference
يقصد فرق الجهد

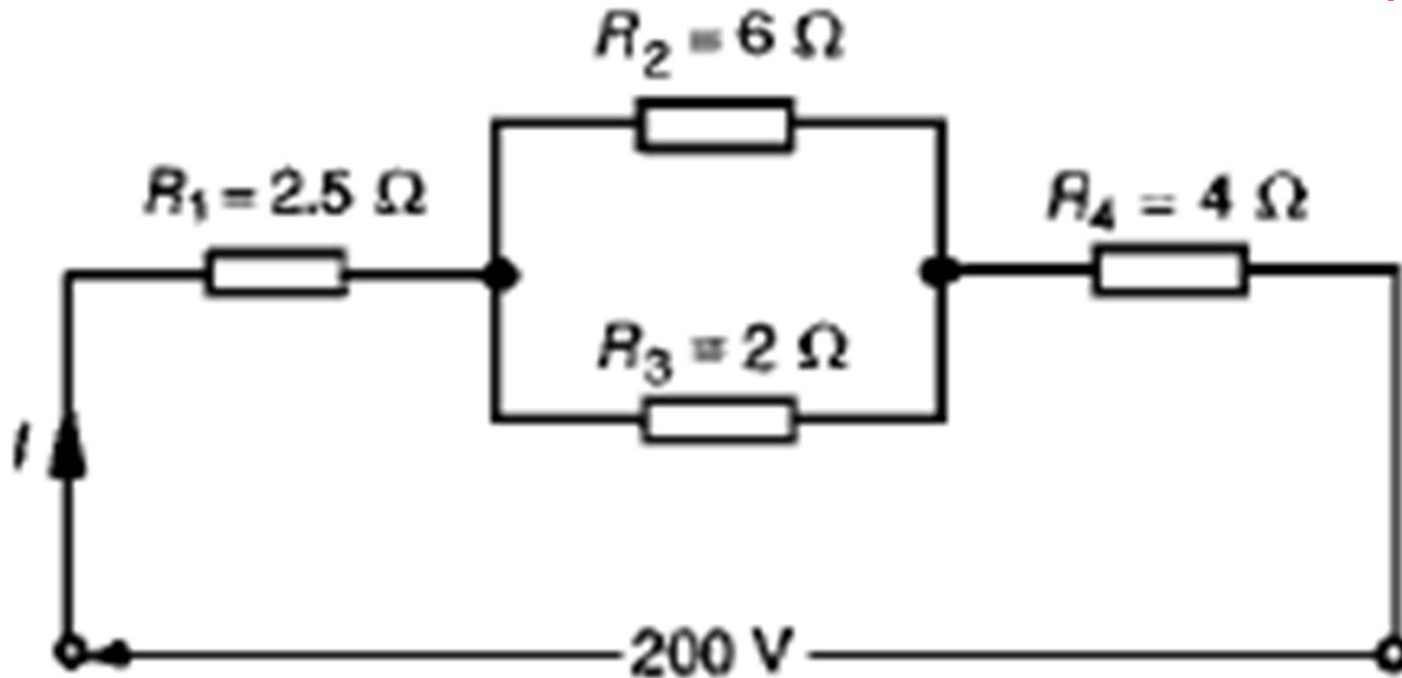


Figure 5.24

- (a) The equivalent resistance R_x of R_2 and R_3 in parallel is:

$$R_x = \frac{6 \times 2}{6 + 2} = 1.5 \Omega$$

The equivalent resistance R_T of R_1 , R_x and R_4 in series is:

$$R_T = 2.5 + 1.5 + 4 = 8 \Omega$$

Supply current

$$I = \frac{V}{R_T} = \frac{200}{8} = 25 \text{ A}$$

- (b) The current flowing through R_1 and R_4 is 25 A.
The current flowing through

$$R_2 = \left(\frac{R_3}{R_2 + R_3} \right) I = \left(\frac{2}{6 + 2} \right) 25$$
$$= \mathbf{6.25 \text{ A}}$$

The current flowing through

$$R_3 = \left(\frac{R_2}{R_2 + R_3} \right) I$$
$$= \left(\frac{6}{6 + 2} \right) 25 = \mathbf{18.75 \text{ A}}$$

p.d. across R_1 , i.e.

$$V_1 = IR_1 = (25)(2.5) = 62.5 \text{ V}$$

p.d. across R_x , i.e.

$$V_x = IR_x = (25)(1.5) = 37.5 \text{ V}$$

p.d. across R_4 , i.e.

$$V_4 = IR_4 = (25)(4) = 100 \text{ V}$$

Hence the p.d. across R_2

$$= \text{p.d. across } R_3 = 37.5 \text{ V}$$

Problem 13. For the circuit shown in Fig. 5.26 calculate (a) the value of resistor R_x such that the total power dissipated in the circuit is 2.5 kW, (b) the current flowing in each of the four resistors.

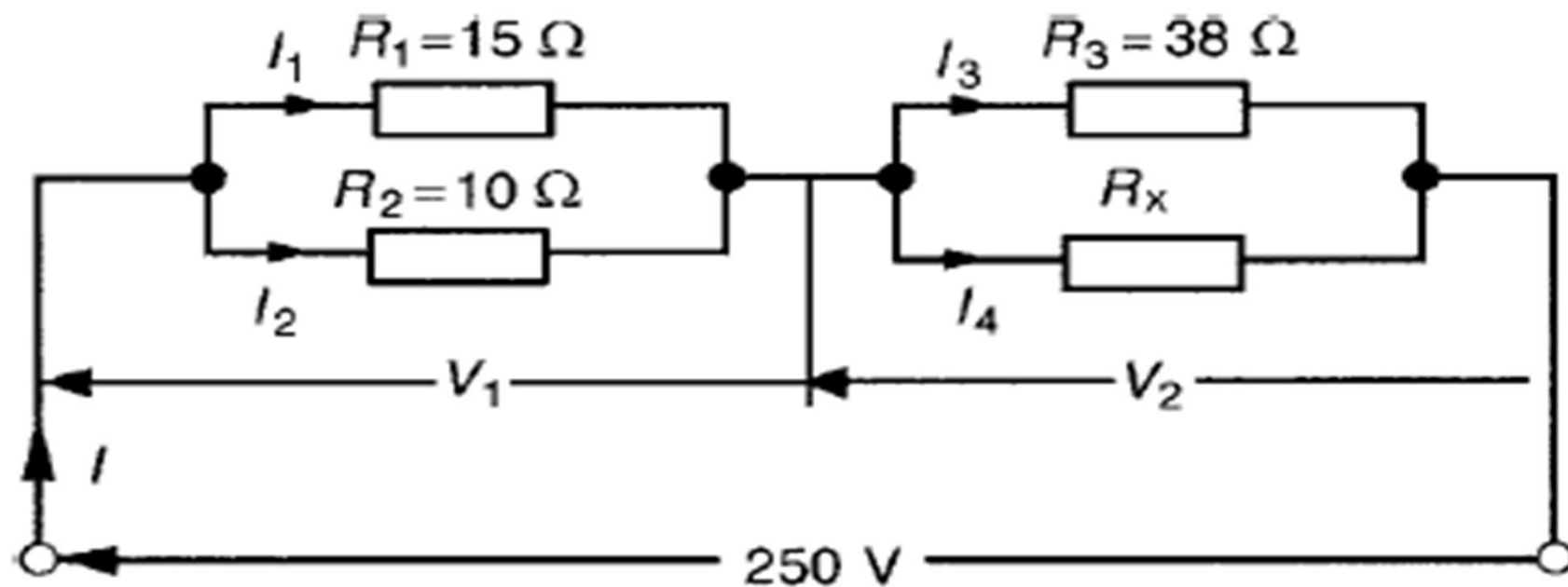


Figure 5.26

(a) Power dissipated $P = VI$ watts, hence
 $2500 = (250)(I)$

$$\text{i.e. } I = \frac{2500}{250} = 10 \text{ A}$$

From Ohm's law,

$$R_T = \frac{V}{I} = \frac{250}{10} = 25 \Omega,$$

where R_T is the equivalent circuit resistance. The equivalent resistance of R_1 and R_2 in parallel is

$$\frac{15 \times 10}{15 + 10} = \frac{150}{25} = 6 \Omega$$

The equivalent resistance of resistors R_3 and R_x in parallel is equal to $25 \Omega - 6 \Omega$, i.e. 19Ω .

The voltage $V_1 = IR$, where R is 6Ω , from above, i.e. $V_1 = (10)(6) = 60 \text{ V}$. Hence

$$V_2 = 250 \text{ V} - 60 \text{ V} = 190 \text{ V}$$

$$= \text{p.d. across } R_3$$

$$= \text{p.d. across } R_x$$

$$I_3 = \frac{V_2}{R_3} = \frac{190}{38} = 5 \text{ A.}$$

Thus $I_4 = 5 \text{ A}$ also, since $I = 10 \text{ A}$. Thus

$$R_x = \frac{V_2}{I_4} = \frac{190}{5} = 38 \Omega$$

Problem 14. For the arrangement shown in Fig. 5.27, find the current I_x .

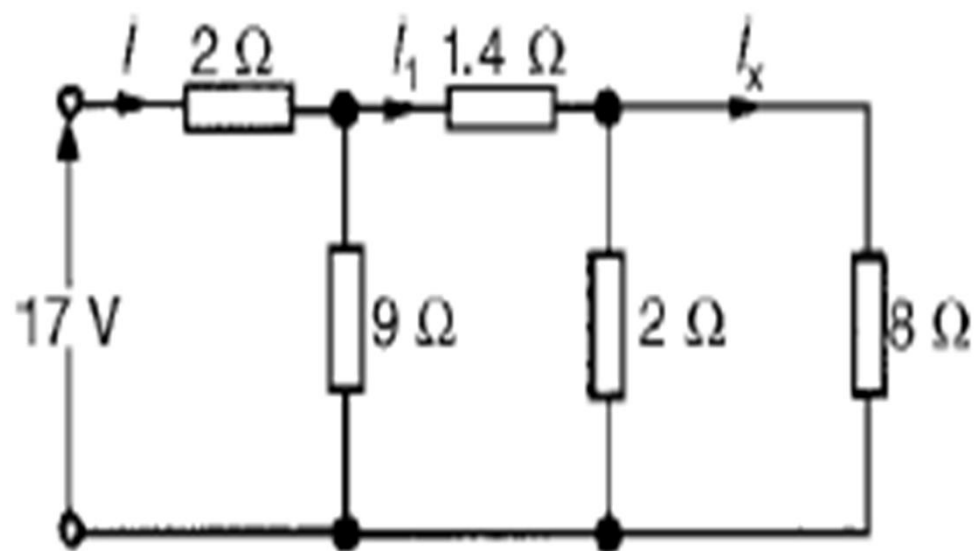


Figure 5.27

$$I = \frac{17}{4.25} = 4 \text{ A}$$

From Fig. 5.28(b),

$$I_1 = \left(\frac{9}{9+3} \right) (I) = \left(\frac{9}{12} \right) (4) = 3 \text{ A}$$

From Fig. 5.27


$$I_x = \left(\frac{2}{2+8} \right) (I_1) = \left(\frac{2}{10} \right) (3) = \mathbf{0.6 \text{ A}}$$

Example – 35 find total Resistance


R_3 , R_4 and R_5 are connected in parallel and their equivalent resistance R is given by

$$\frac{1}{R} = \frac{1}{3} + \frac{1}{6} + \frac{1}{18} = \frac{6 + 3 + 1}{18} = \frac{10}{18}$$

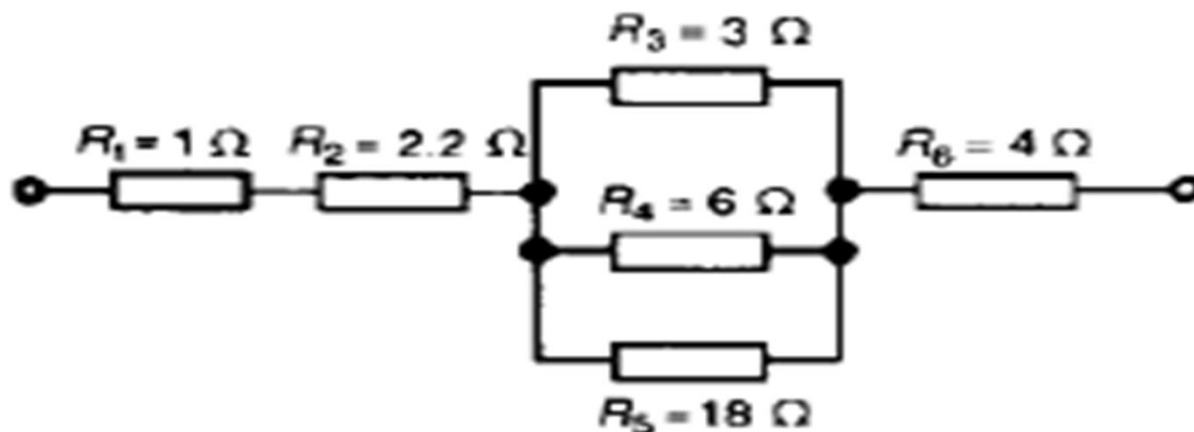
hence $R = (18/10) = 1.8 \Omega$. The circuit is now equivalent to four resistors in series and the equivalent circuit resistance = $1 + 2.2 + 1.8 + 4 = 9 \Omega$



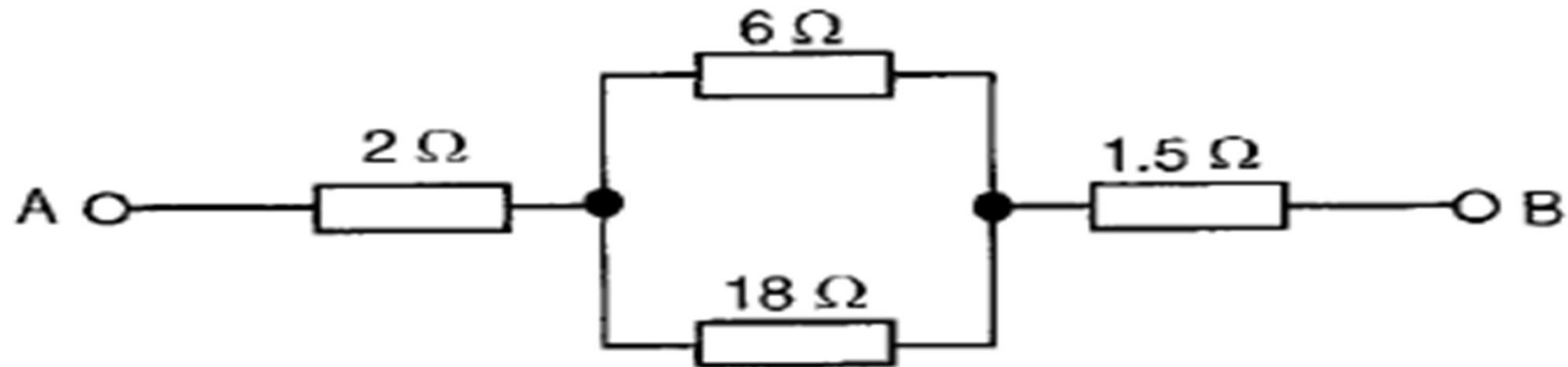Example :36 Find the total Resistance (H.W)




(a)

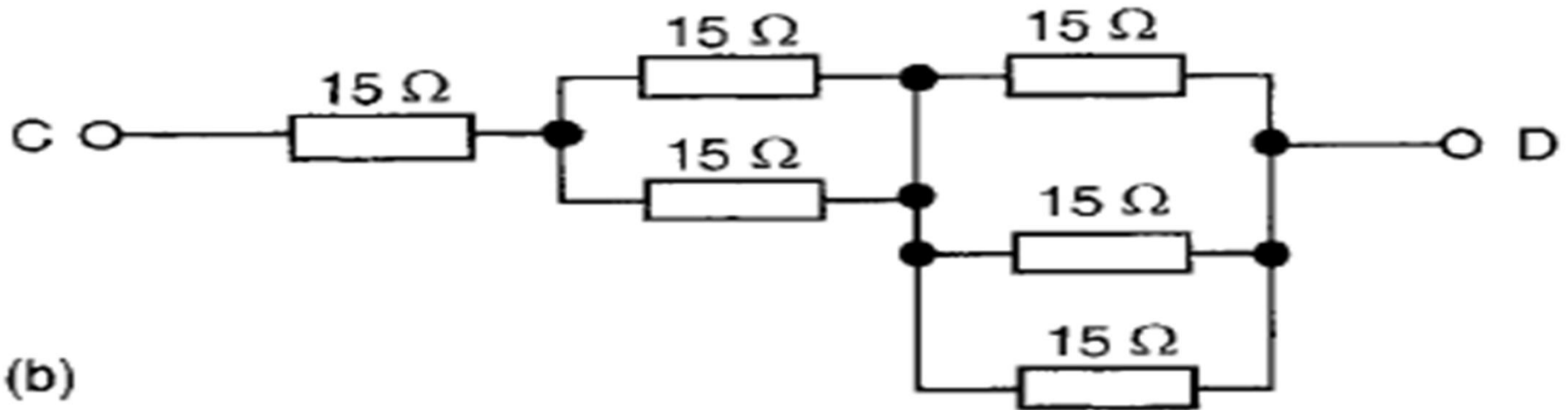


(b)

Example : 37 Determine the currents and voltages indicated in fig:

[H W]

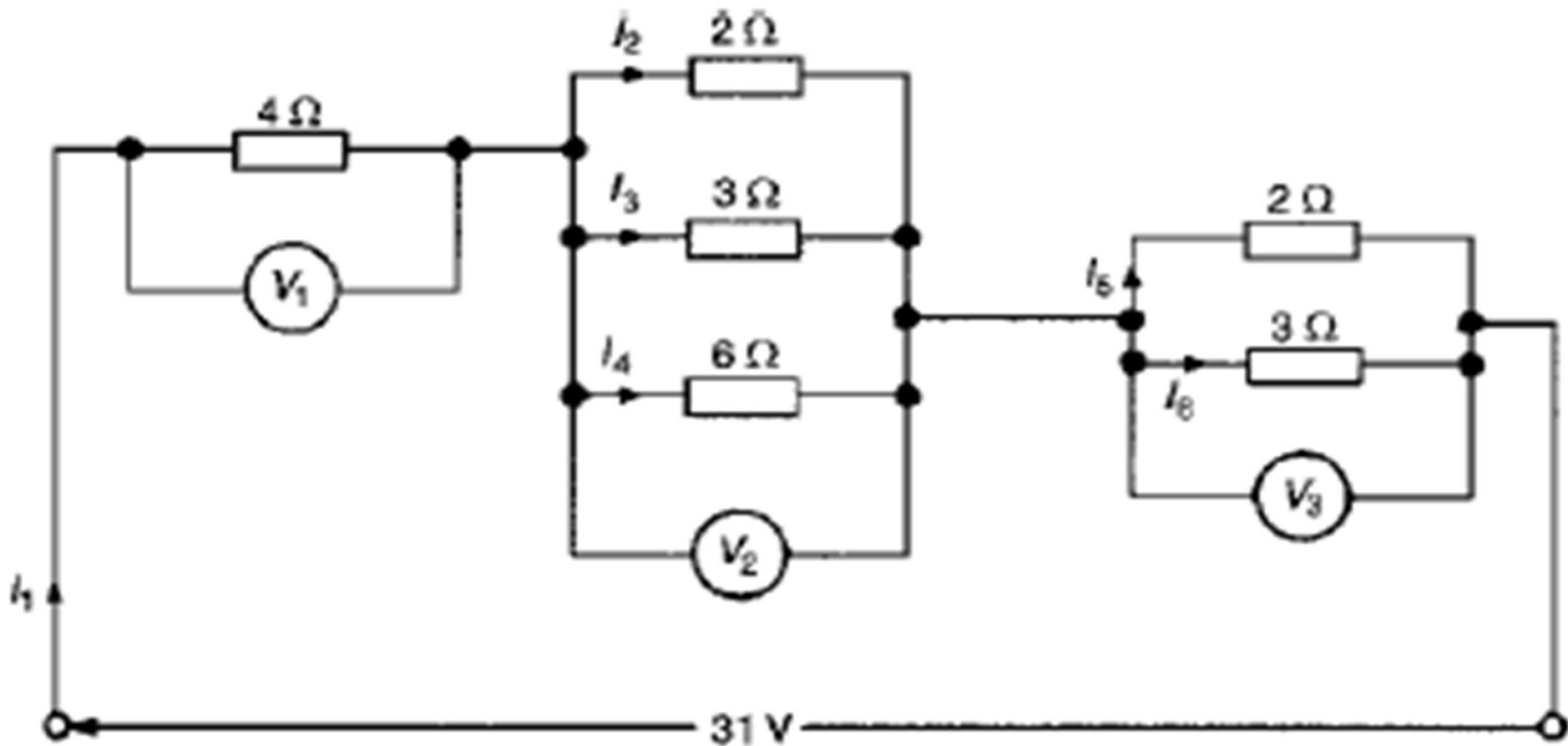

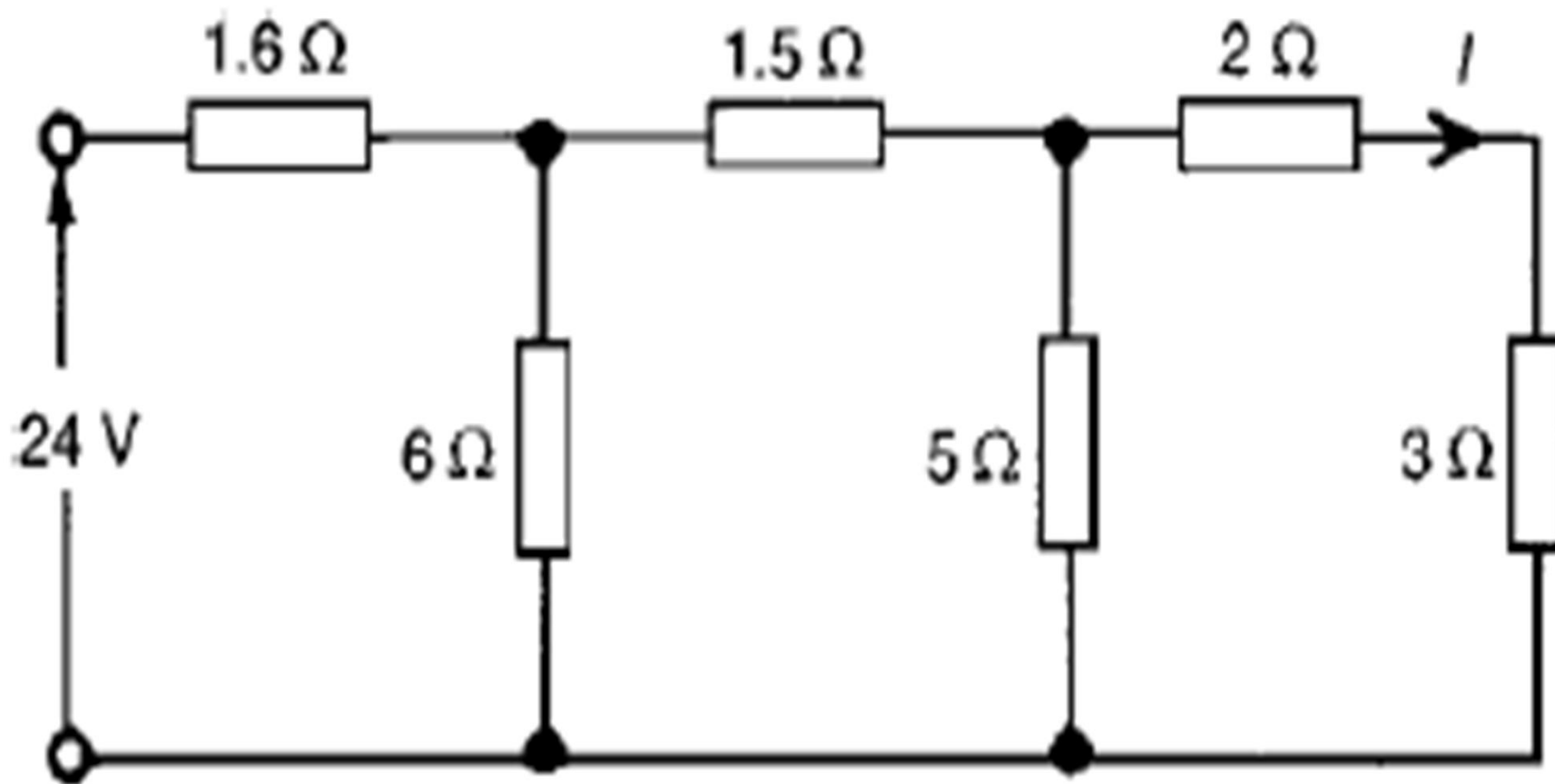
**Example : 38 find the current (I)
in fig . Shown:(H.W)**



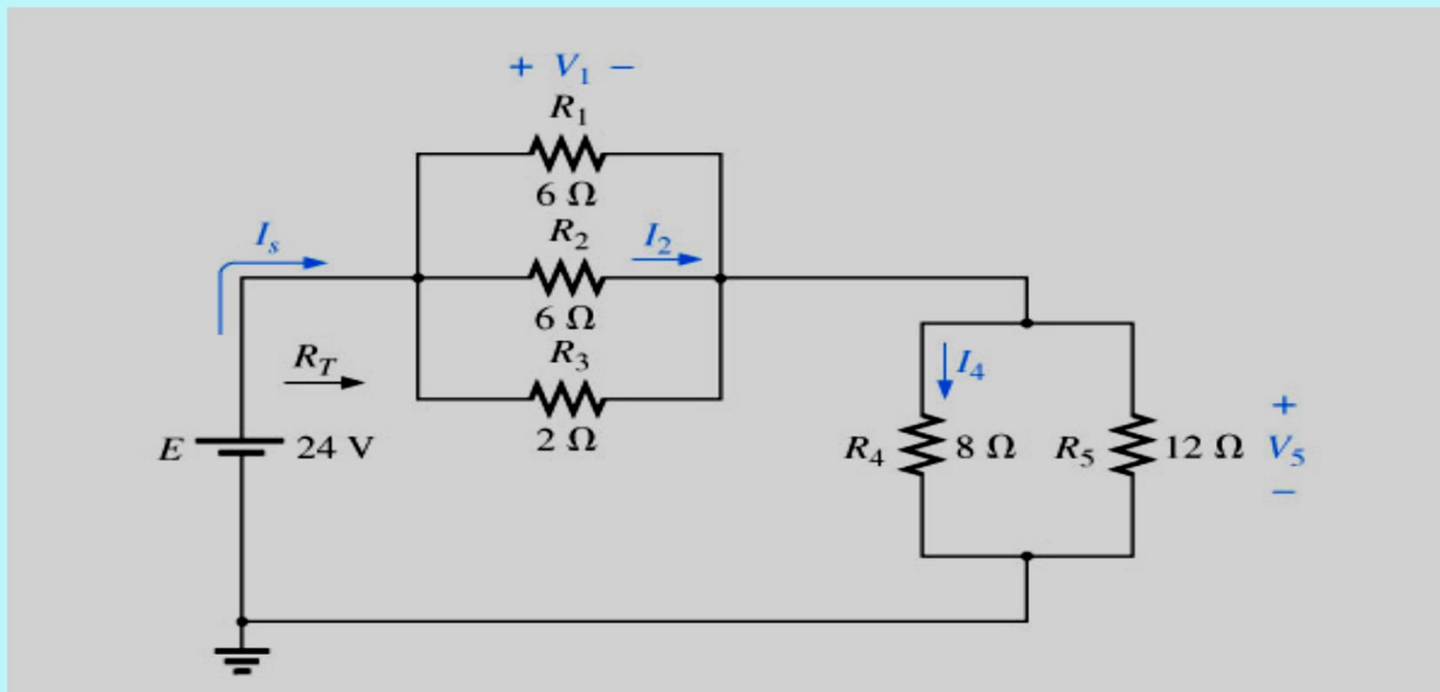Example – 39

H.W


Find the indicated currents and voltages for the network shown in Fig.



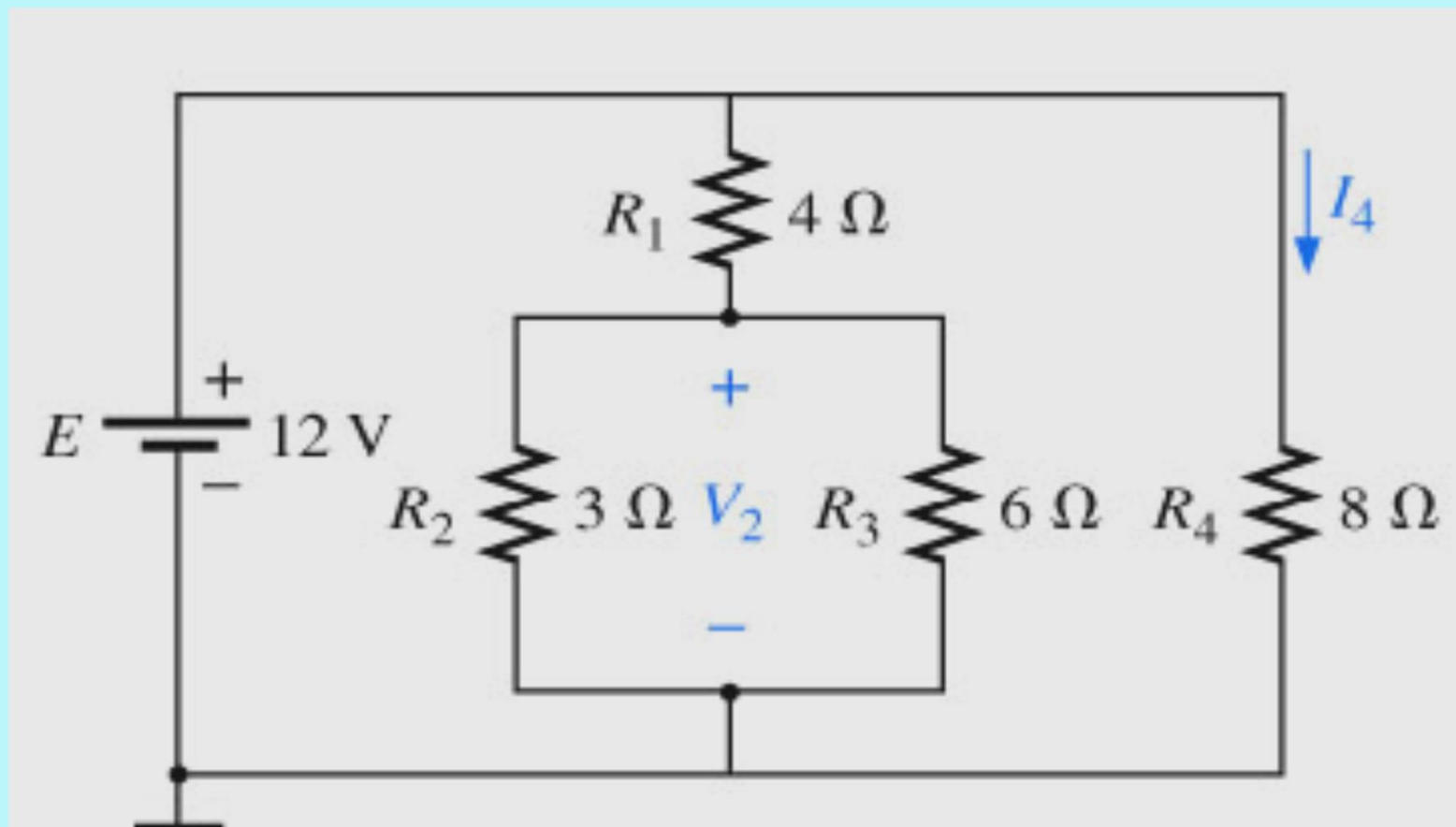Example – 40

H.W


- ⚡ Find the current I_4 and the voltage V_2 for the network shown in fig .



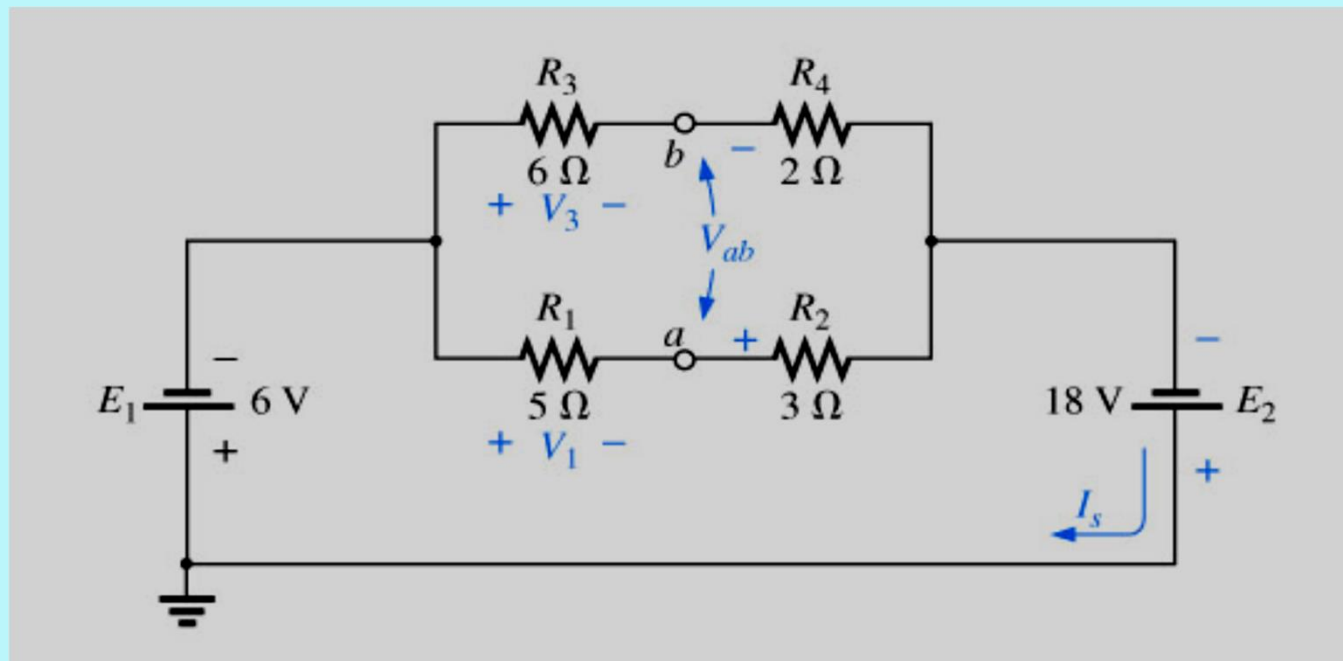Example – 41

H.W

- Find the voltages V_1 , V_2 and V_{ab} for the network in Fig.
- Calculate the source current I_s .



Example – 42

H.W

Calculate the indicated currents and voltage in Fig.

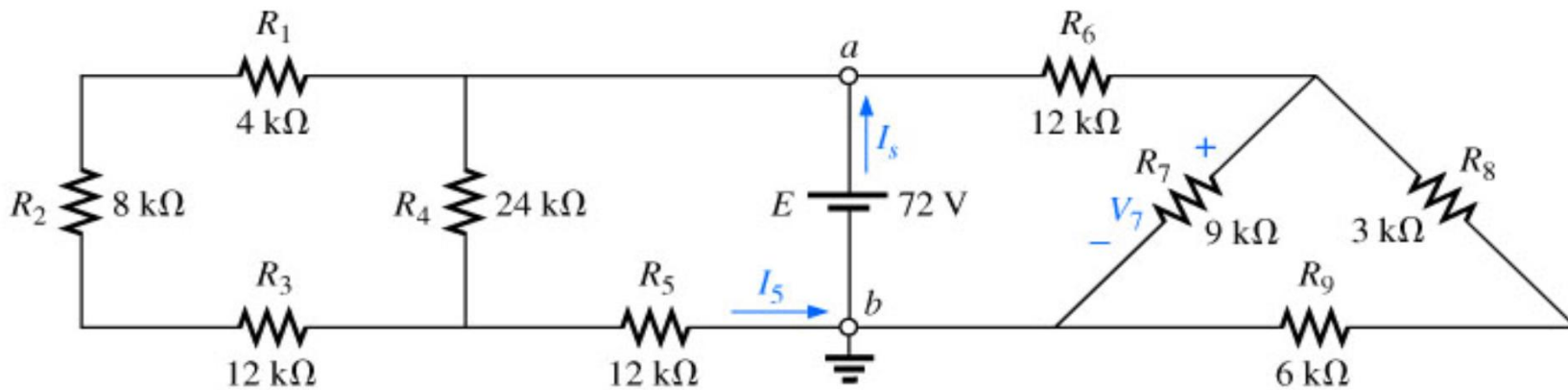


FIG. 7.22

Example 7.9.