

Electrical Circuit

Kirchhoff's Laws

الافكار المركبة

1 - Definitions

2 - kirchhoff,s current Law (KCL)



3 - Kirchhoff,s Voltage Law (KVL)

4 - Examples

5 - Home works

Kirchhoff's Current Law

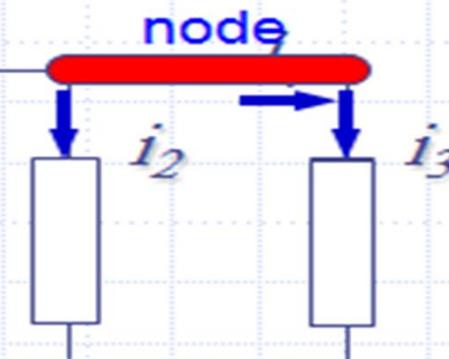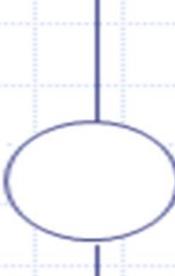- The sum of currents flowing **into** a node must be balanced by the sum of currents flowing **out of** the node.



i_1 flows **into** the node

i_2 flows **out** of the node

i_3 flows **out** of the node


$$i_1 = i_2 + i_3$$

$$\sum i = 0$$

Example 1: Kirchhoff's Current Law:

Q: How much is the current I_o ?

A: $i_o = 2.5 \text{ mA} + 4 \text{ mA} = 6.5 \text{ mA}$

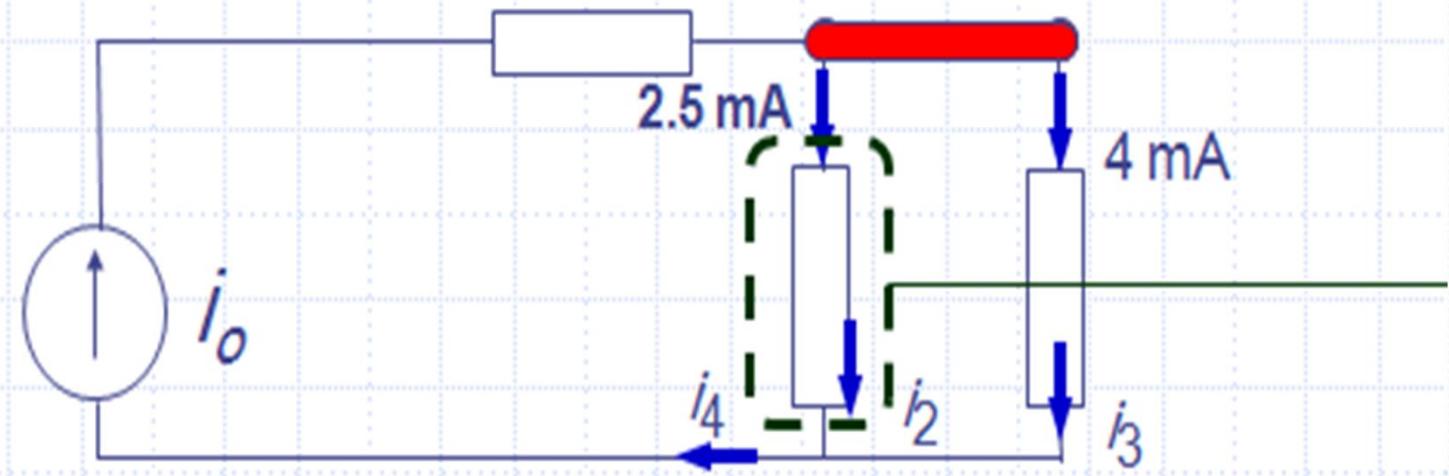


Example 2: Kirchhoff's Current Law:

Q: How much are the currents i_1 and i_2 ?

A: $i_2 = 10 \text{ mA} - 3 \text{ mA} = 7 \text{ mA}$

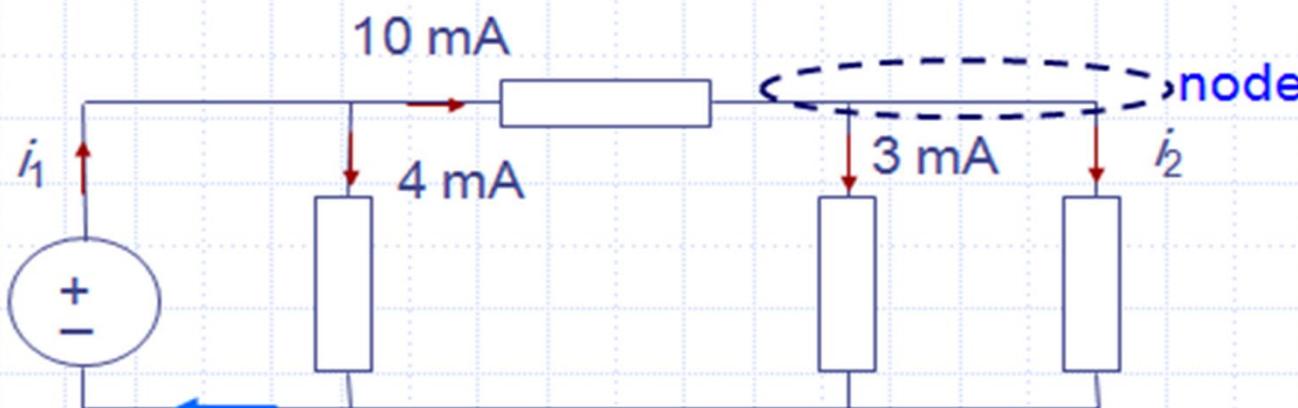$i_1 = 10 \text{ mA} + 4 \text{ mA} = 14 \text{ mA}$




$$4 \text{ mA} + 3 \text{ mA} + 7 \text{ mA} = 14 \text{ mA}$$

Kirchhoff's Voltage Law:

$$v_1 = v_2 + v_3$$

- This equation can also be written in the following form:

$$-v_1 + v_2 + v_3 = 0$$

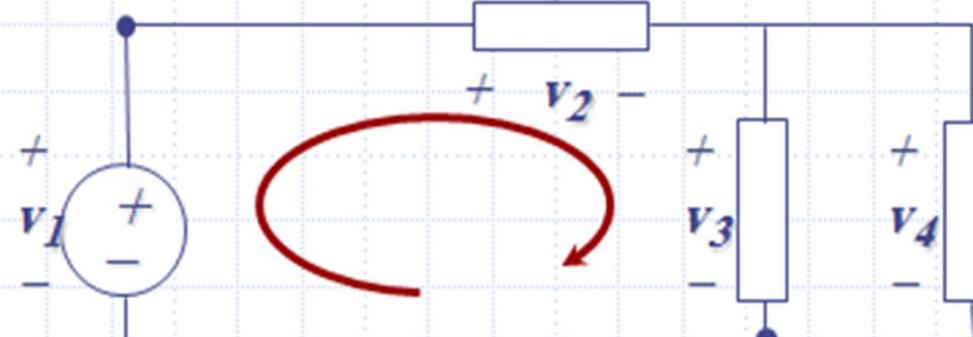


A formal statement of **Kirchhoff's Voltage Law**:

The sum of voltages around a **closed loop** is zero.

Example 1: Kirchhoff's Voltage Law:

Q: How much is the voltage V_o ?

A: $V_o = 3.1 \text{ V} + 6.8 \text{ V}$

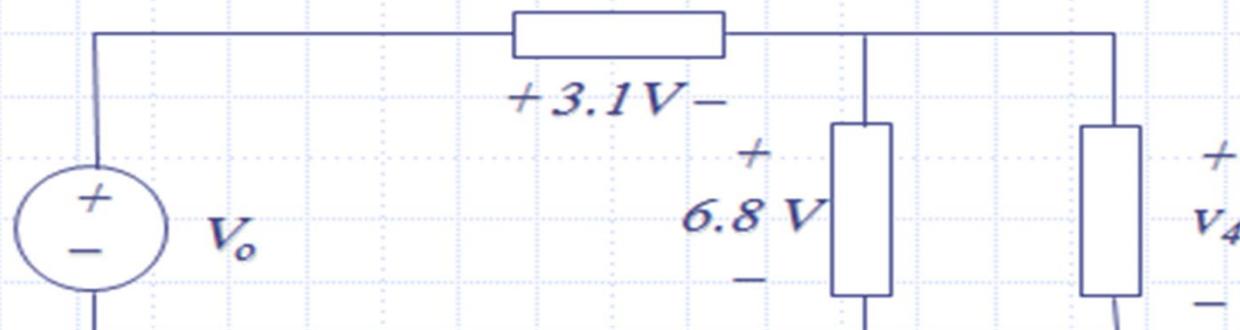

Q: How much is the voltage v_4 ?

A: $v_4 = 6.8 \text{ V}$

Example 2: Kirchhoff's Voltage Law:


Q: If $v_1 = 10 \text{ V}$ and $v_5 = 2 \text{ V}$, what are v_2 , v_3 , and v_4 ?

A:


$$v_2 = 10 \text{ V}$$


$$v_3 = 10 \text{ V} - 2 \text{ V} = 8 \text{ V}$$

$$v_4 = 2 \text{ V}$$

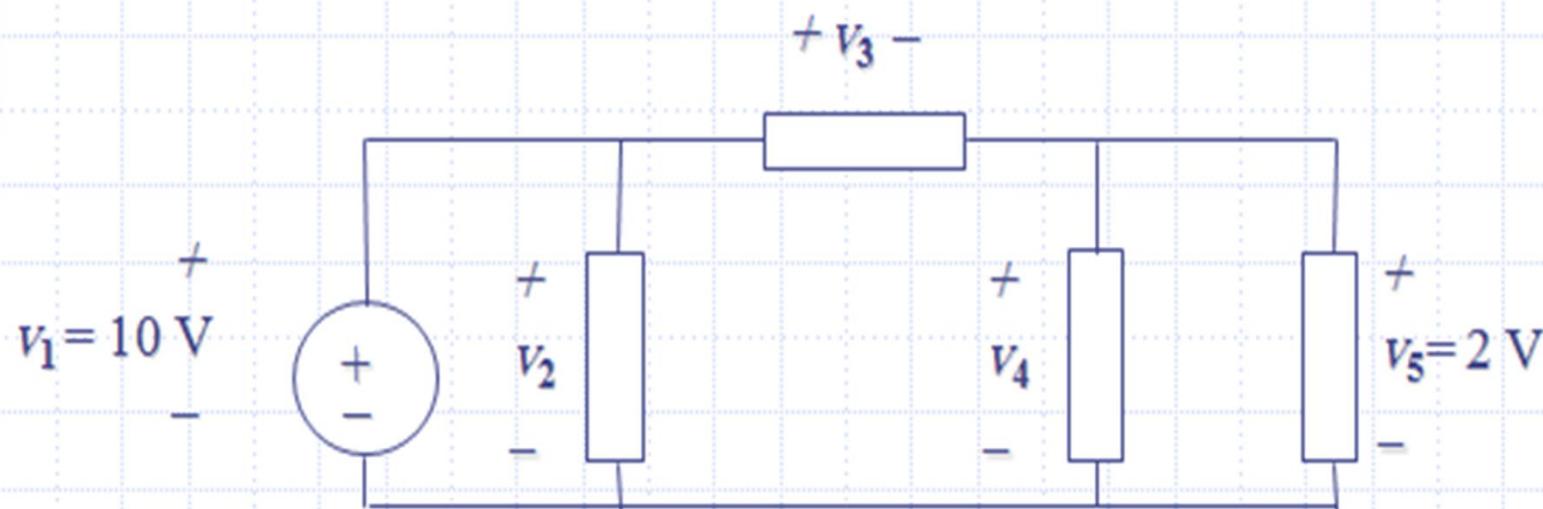

Example: 3 find loop currents

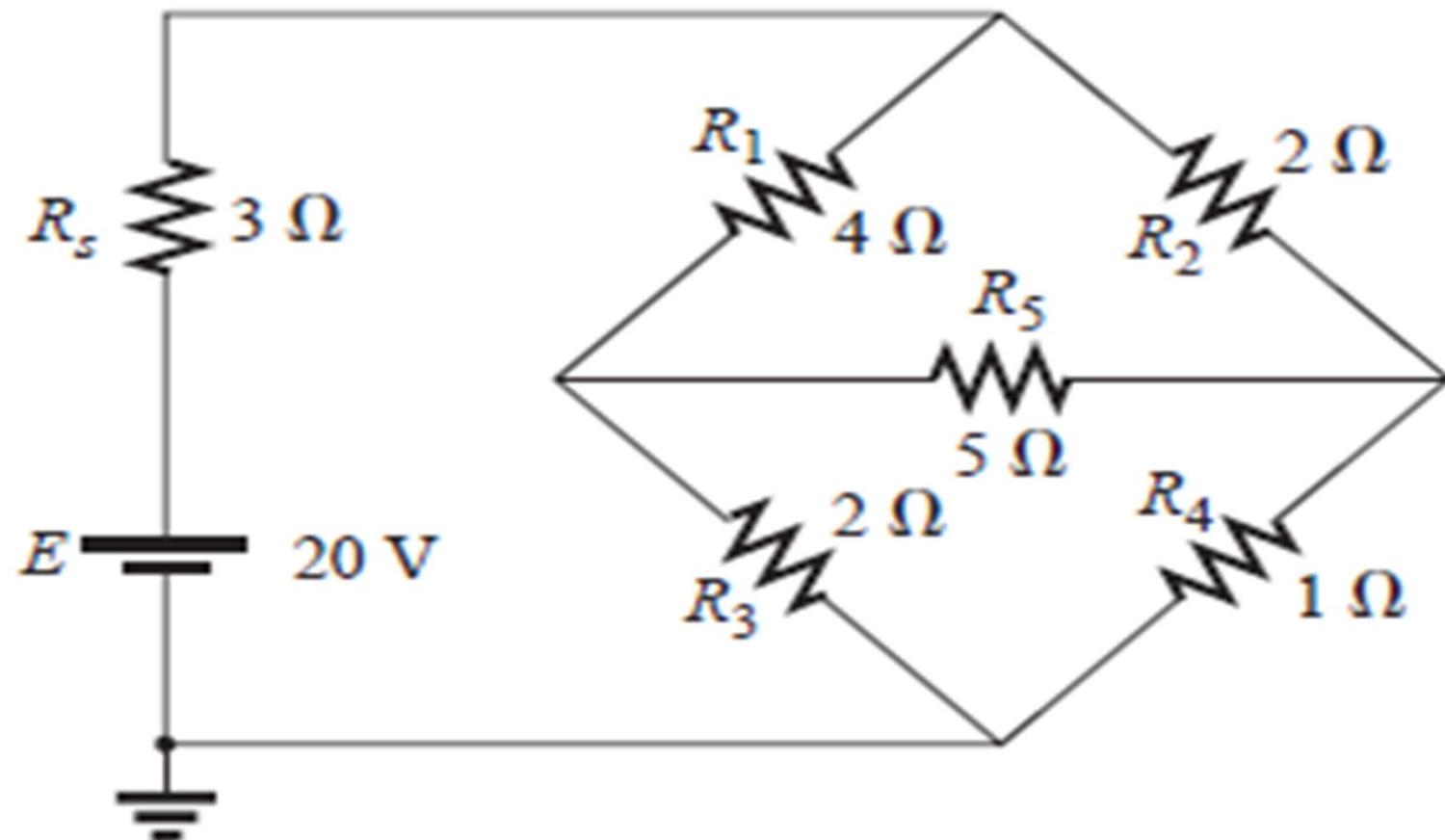

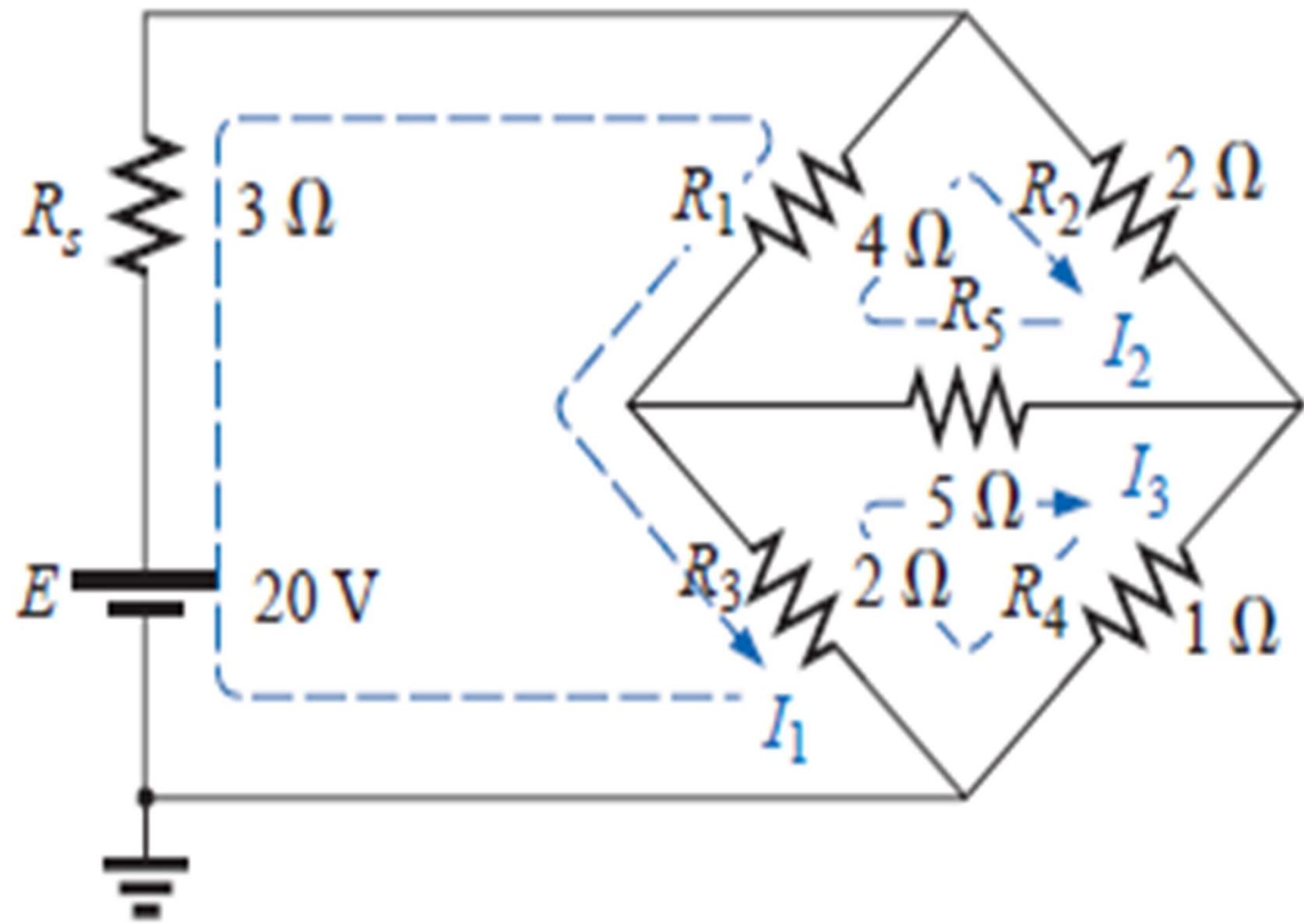

$$\begin{array}{r}
 (3\Omega + 4\Omega + 2\Omega)I_1 - (4\Omega)I_2 - (2\Omega)I_3 = 20\text{ V} \\
 (4\Omega + 5\Omega + 2\Omega)I_2 - (4\Omega)I_1 - (5\Omega)I_3 = 0 \\
 \hline
 (2\Omega + 5\Omega + 1\Omega)I_3 - (2\Omega)I_1 - (5\Omega)I_2 = 0
 \end{array}$$

and

$$\begin{array}{r}
 9I_1 - 4I_2 - 2I_3 = 20 \\
 -4I_1 + 11I_2 - 5I_3 = 0 \\
 \hline
 -2I_1 - 5I_2 + 8I_3 = 0
 \end{array}$$

with the result that

$$I_1 = 4\text{ A}$$


$$I_2 = 2.667\text{ A}$$

$$I_3 = 2.667\text{ A}$$

The net current through the $5\text{-}\Omega$ resistor is

$$I_{5\Omega} = I_2 - I_3 = 2.667\text{ A} - 2.667\text{ A} = 0\text{ A}$$

Example: 4 find branch currents

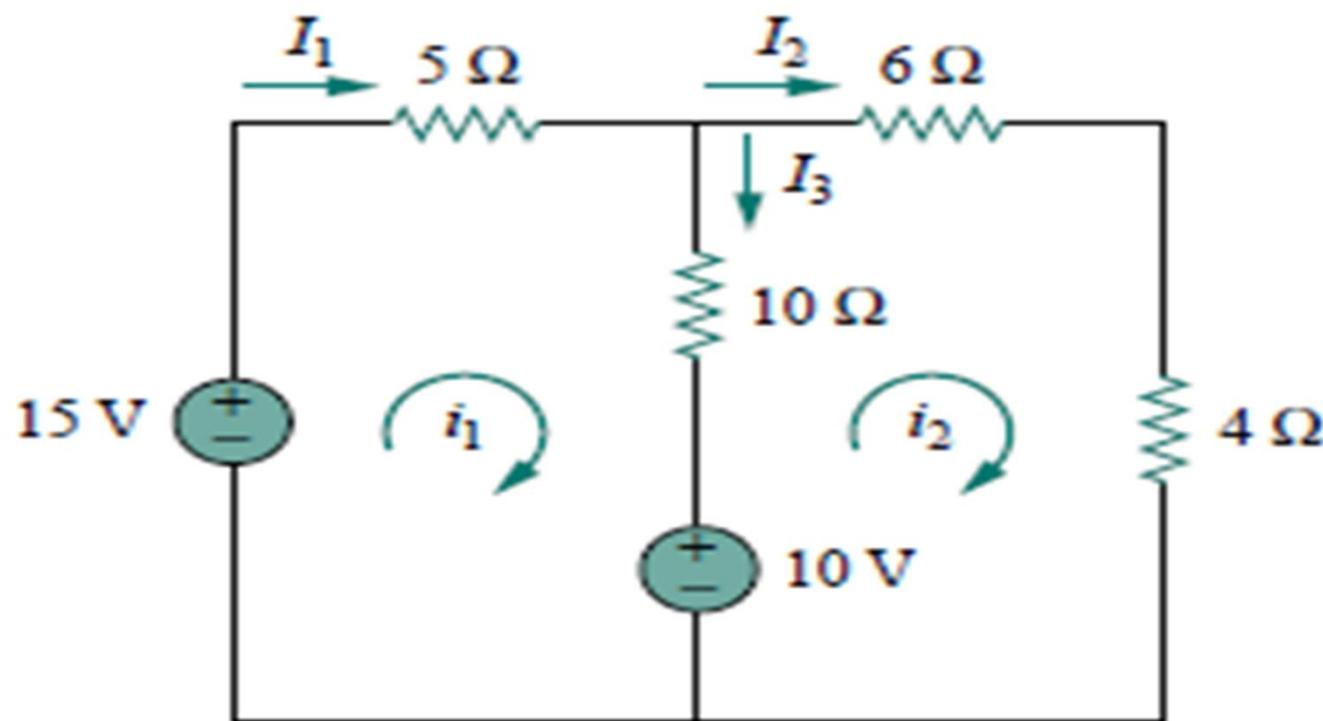

Solution:

We first obtain the mesh currents using KVL. For mesh 1,

$$-15 + 5i_1 + 10(i_1 - i_2) + 10 = 0$$

or

$$3i_1 - 2i_2 = 1 \quad (3.5.1)$$

For mesh 2,

$$6i_2 + 4i_2 + 10(i_2 - i_1) - 10 = 0$$

or

$$i_1 = 2i_2 - 1 \quad (3.5.2)$$

METHOD I Using the substitution method, we substitute Eq. (3.5.2) into Eq. (3.5.1), and write

$$6i_2 - 3 - 2i_2 = 1 \quad \Rightarrow \quad i_2 = 1 \text{ A}$$

From Eq. (3.5.2), $i_1 = 2i_2 - 1 = 2 - 1 = 1 \text{ A}$. Thus,

$$I_1 = i_1 = 1 \text{ A}, \quad I_2 = i_2 = 1 \text{ A}, \quad I_3 = i_1 - i_2 = 0$$

METHOD 2 To use Cramer's rule, we cast Eqs. (3.5.1) and (3.5.2) in matrix form as

$$\begin{bmatrix} 3 & -2 \\ -1 & 2 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} 1 \\ 1 \end{bmatrix}$$

We obtain the determinants

$$\Delta = \begin{vmatrix} 3 & -2 \\ -1 & 2 \end{vmatrix} = 6 - 2 = 4$$

$$\Delta_1 = \begin{vmatrix} 1 & -2 \\ 1 & 2 \end{vmatrix} = 2 + 2 = 4, \quad \Delta_2 = \begin{vmatrix} 3 & 1 \\ -1 & 1 \end{vmatrix} = 3 + 1 = 4$$


Thus,

$$i_1 = \frac{\Delta_1}{\Delta} = 1 \text{ A}, \quad i_2 = \frac{\Delta_2}{\Delta} = 1 \text{ A}$$

as before.


Example: 5 - find loop currents

H.W -1

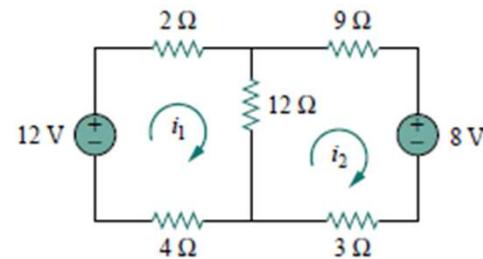

Example: 6 - find i_o , ($H.W - 2$)


V_{ab}

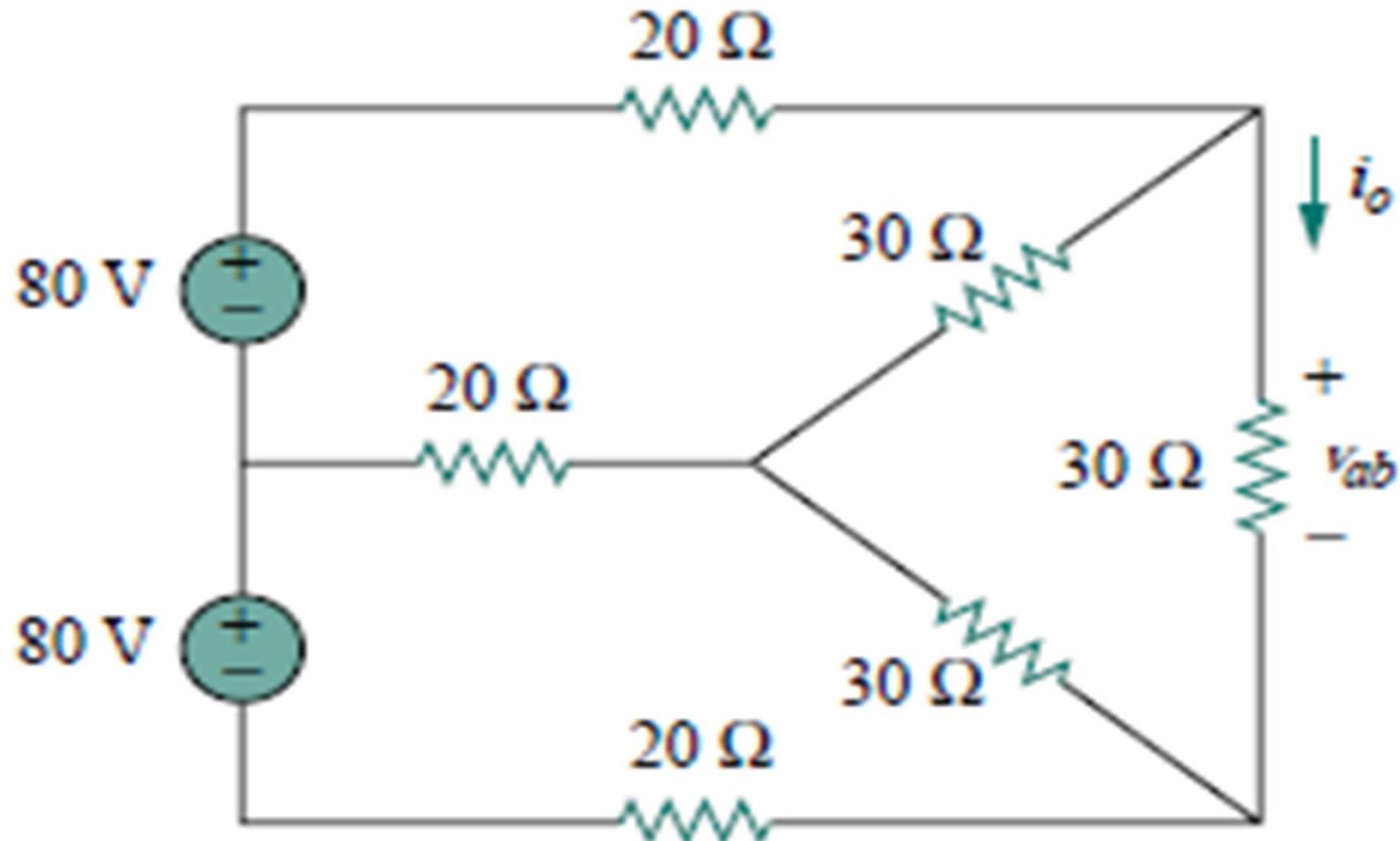

Example : 7 - find the magnitude and the directions of the unknown current


$$I_1 = 5 - 2 = 3 \text{ A}$$

$$I_2 = 4 - I_1 = 4 - 3 = 1 \text{ A}$$

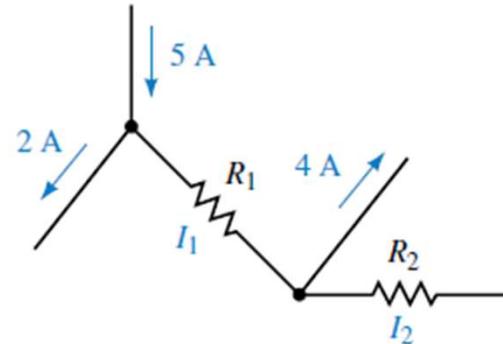


(a)

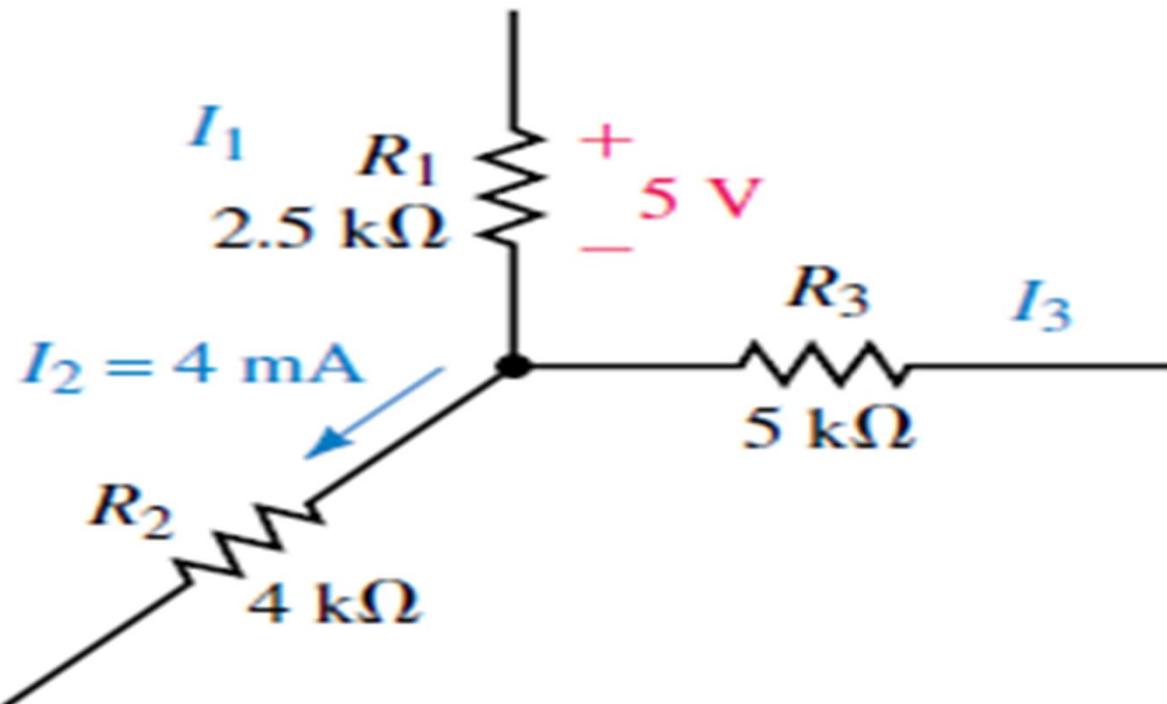
Example : 8 - find the magnitude
and the directions of the unknown
current (H.W-3)-



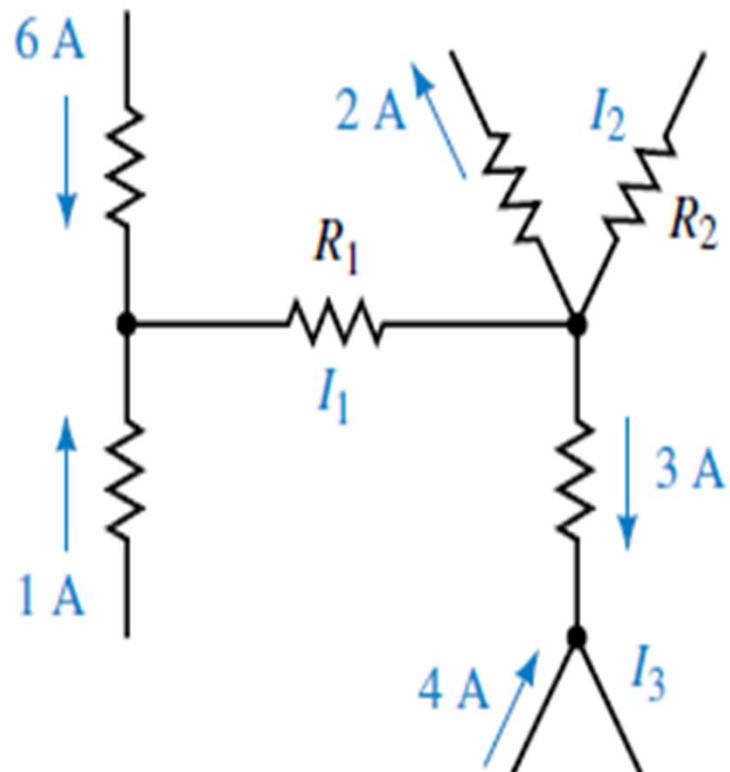Example : 9 - find the magnitude and the directions of the unknown currents(H.W-4)




(b)

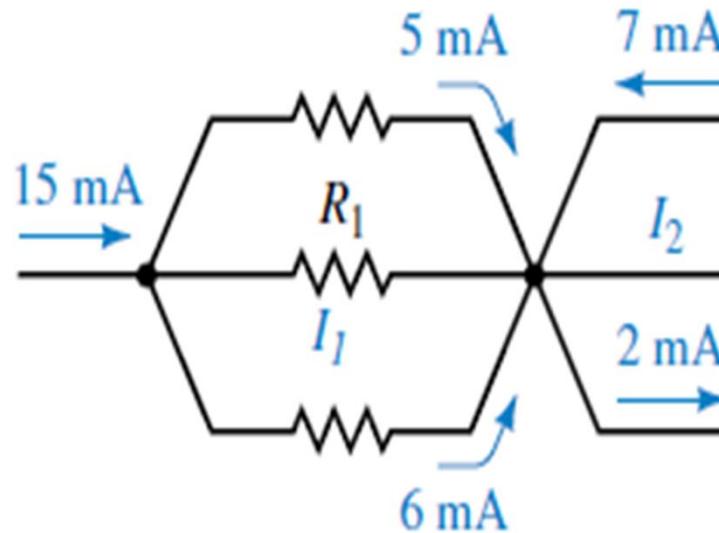


(c)

Example : 10- find the magnitude and the directions of the unknown current and voltage


H.W-5

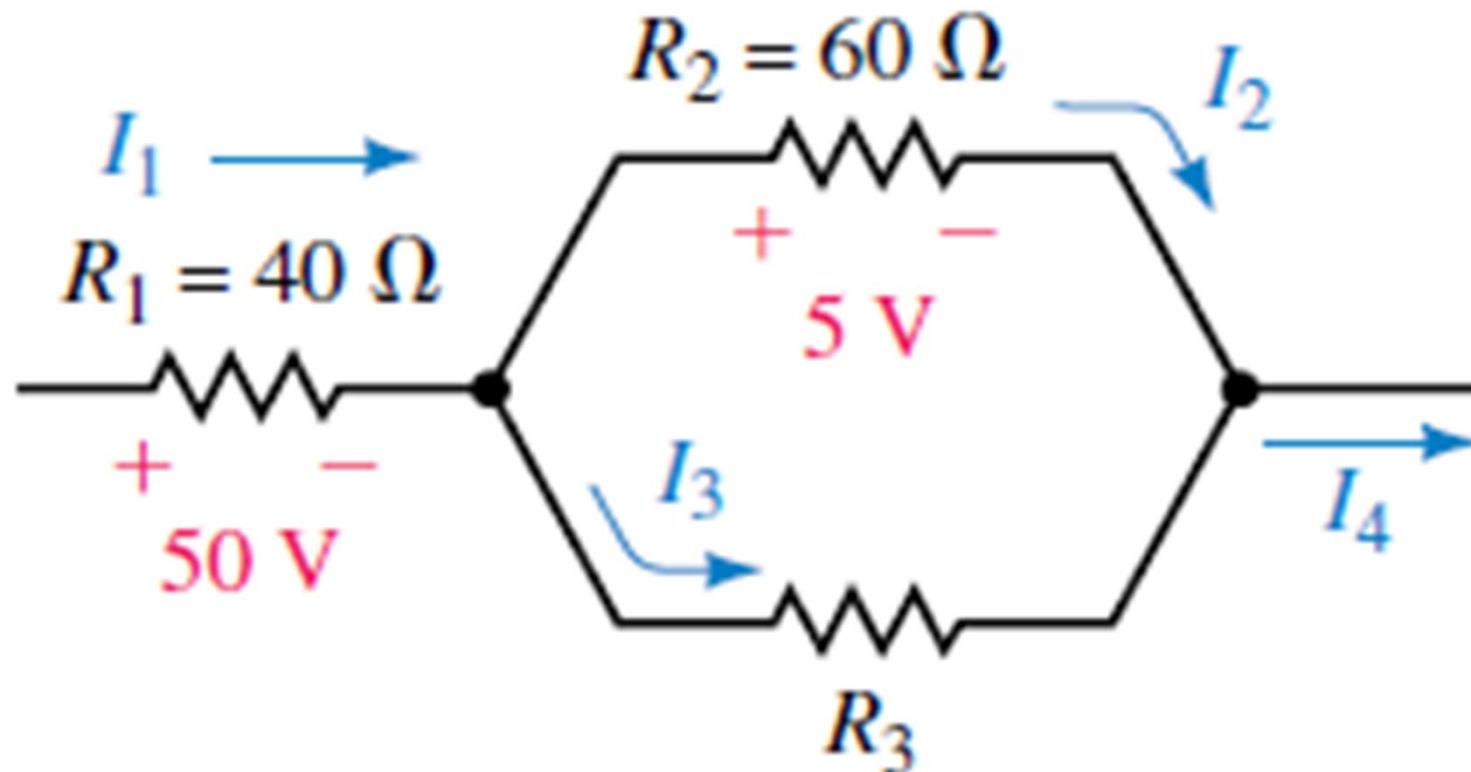

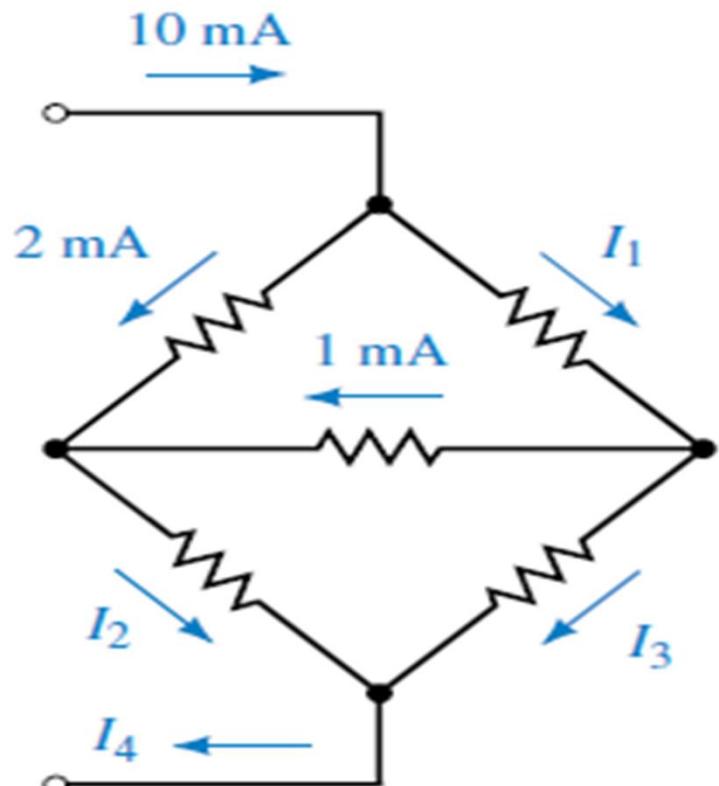and the directions of the unknown current(H.W-6)




(a)

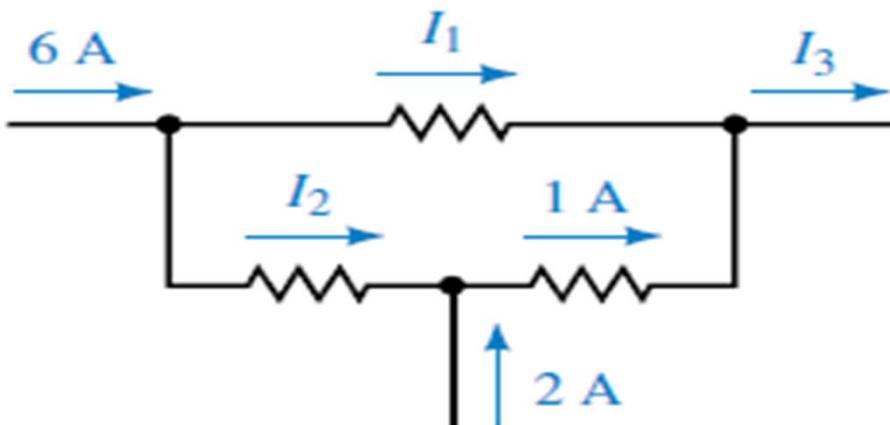


(b)

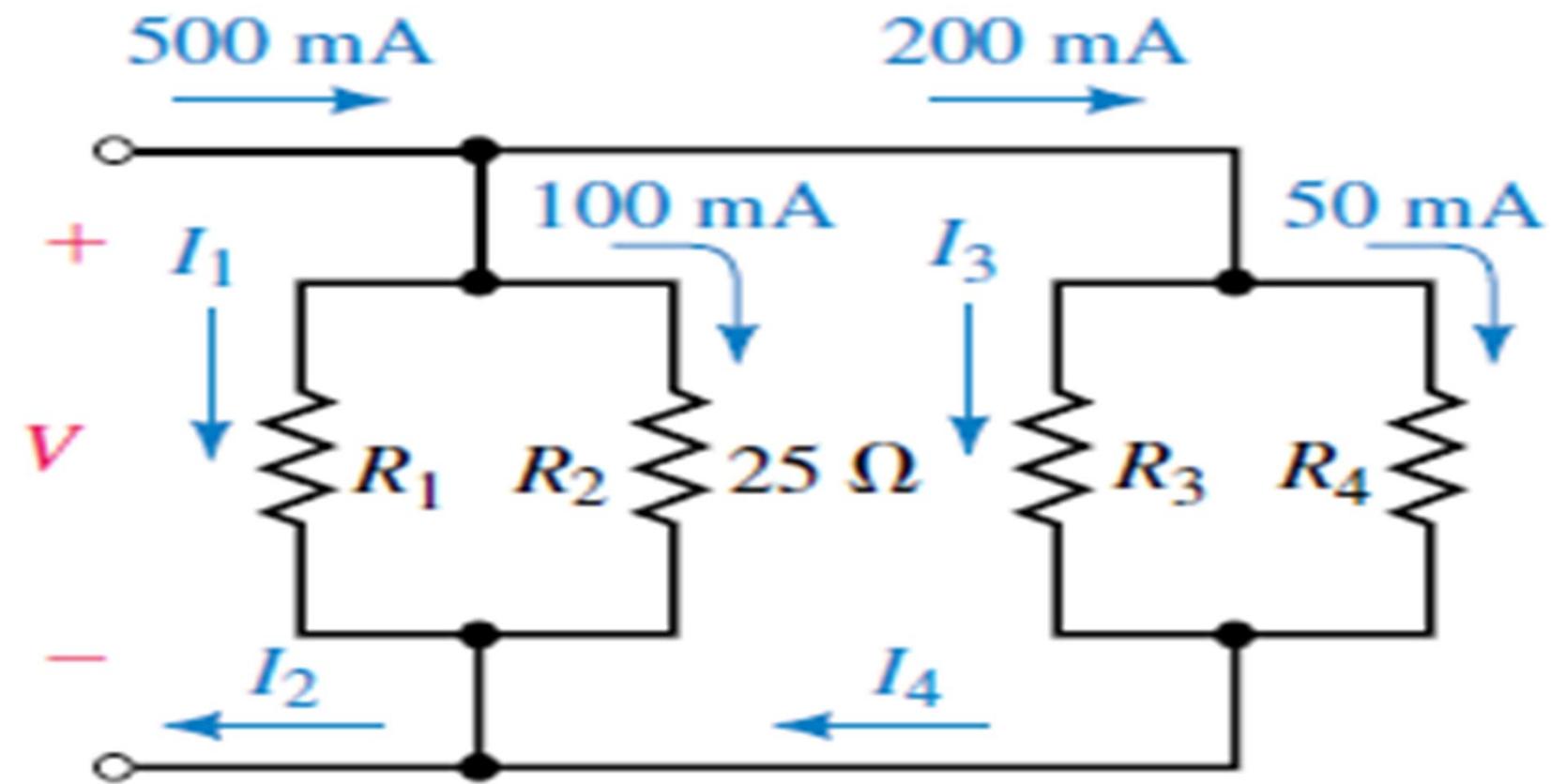
Example : 12 - find the magnitude and the directions of the unknown current and voltage(h.w -7)



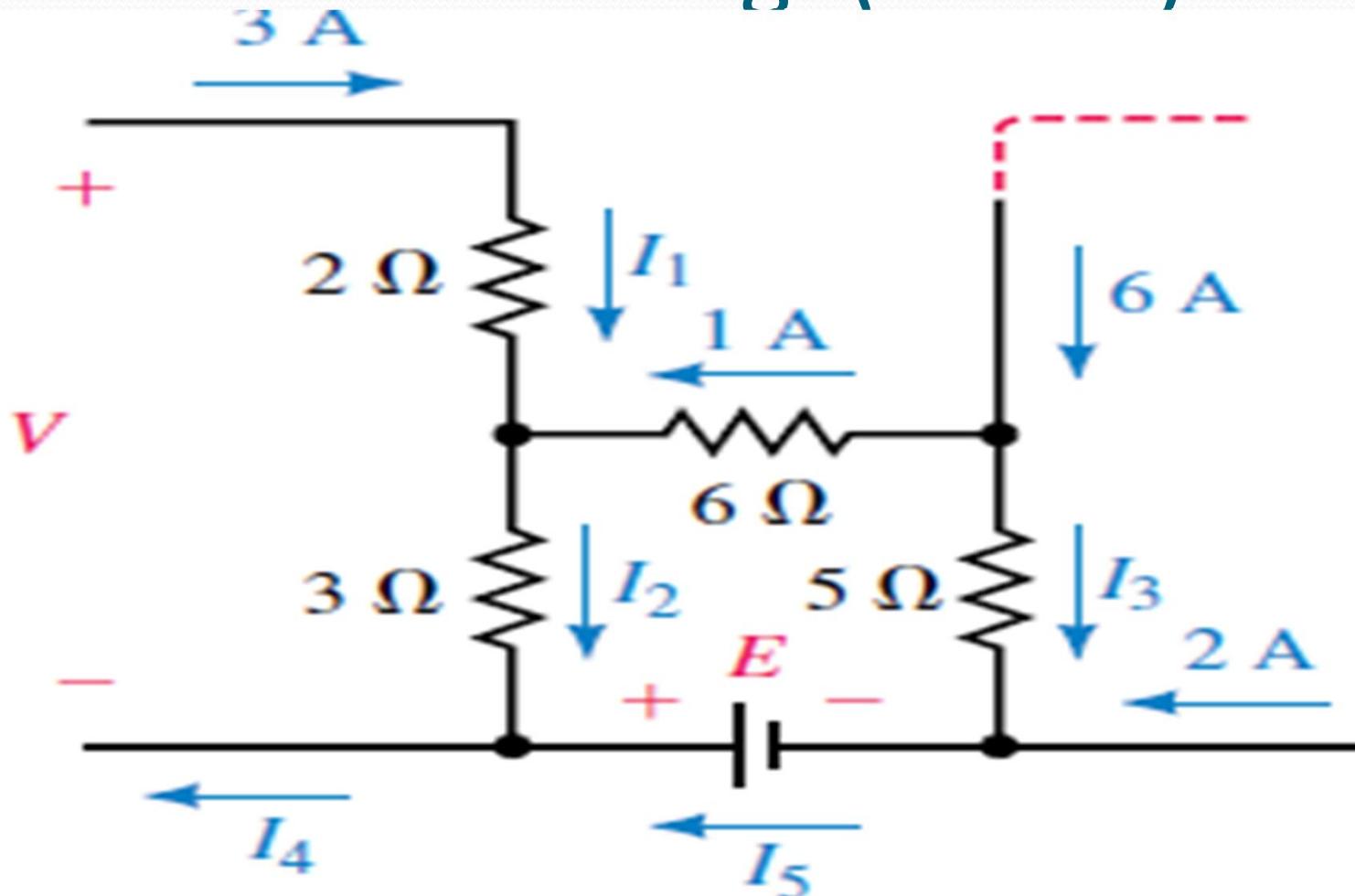
Example : 13 - find the magnitude and the directions of the unknown current and voltage(H.W-8)



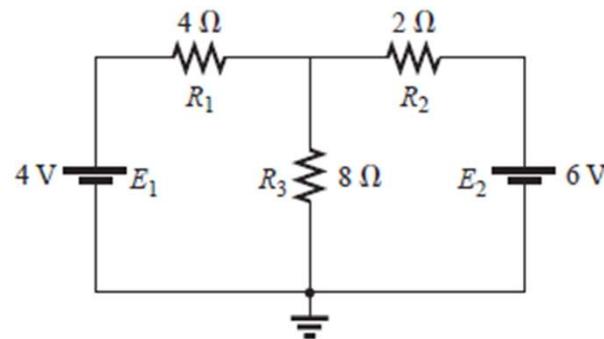
Example : 14 - for the circuit H. 5
find the branch currents()shown



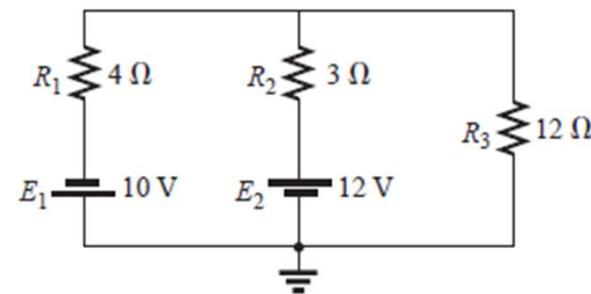
Example :15 - for the circuit shown
find the branch currents(h.w-10)



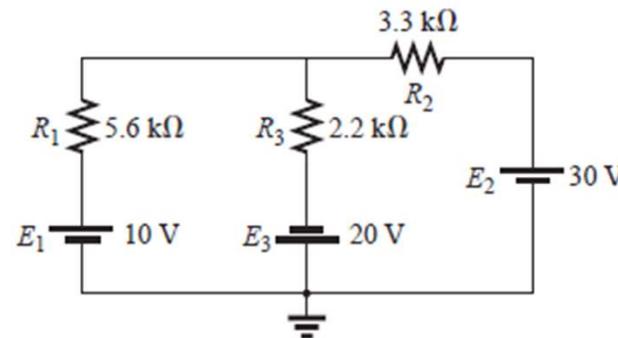
Example : 16 - for the circuit shown find the branch currents



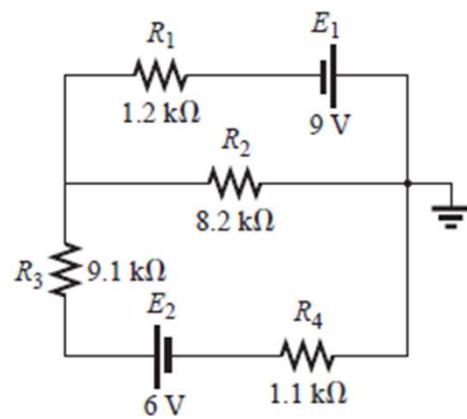
Example :17 - for the circuit shown
find the branch currents



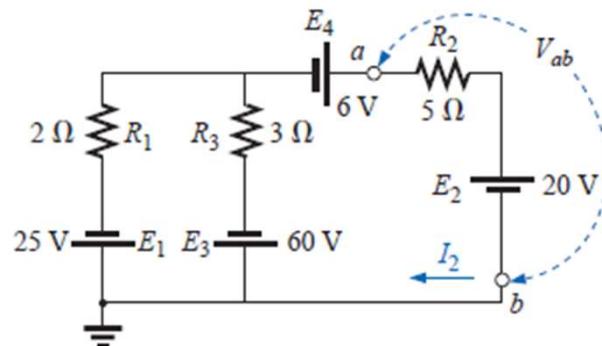Example : 18 - for the circuit shown
find the branch currents and V_{ab}



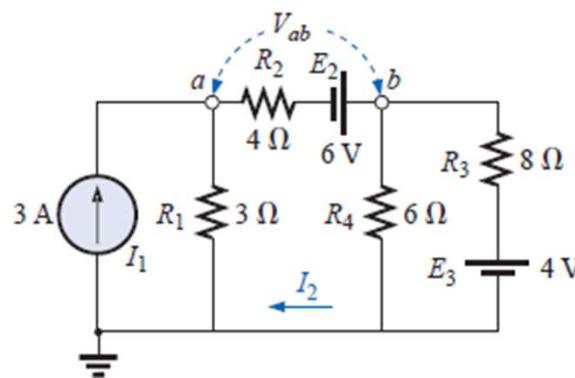Example : 19 - for the circuit
the branch currents shown find
and V_{ab}



Example : 20 - for the circuit shown
find the branch currents and V_a

